

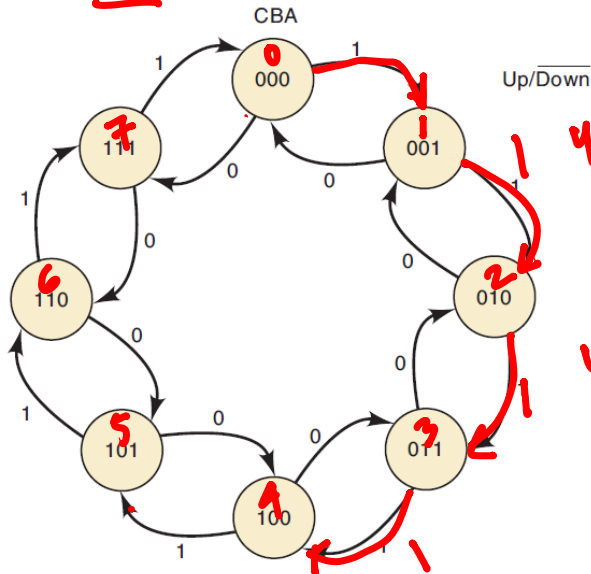
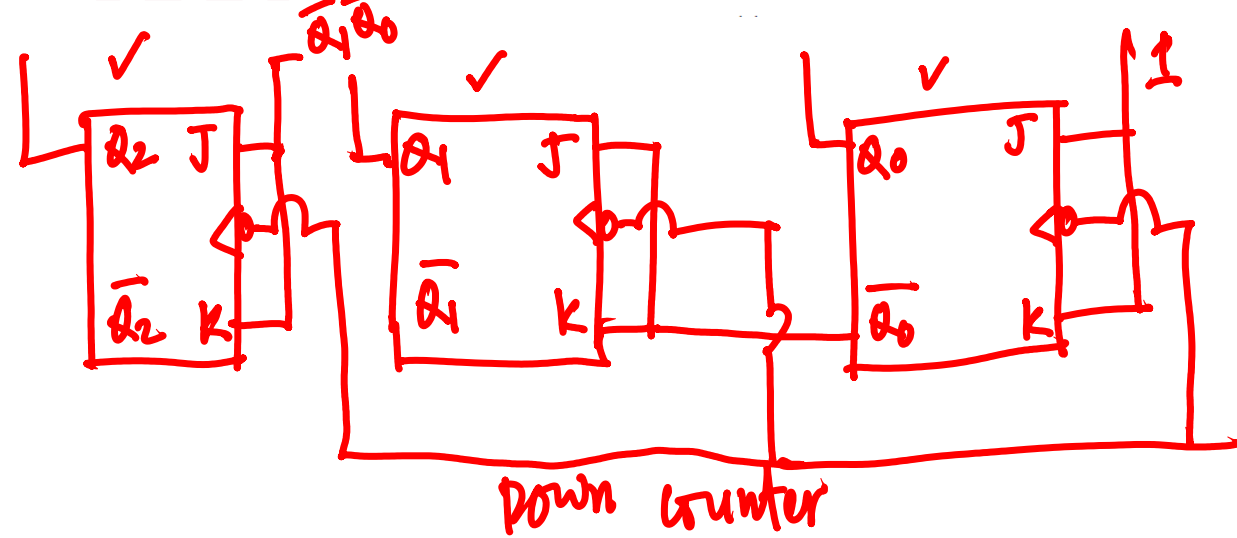


COUNTER CIRCUIT

- Synchronous up/down counter:

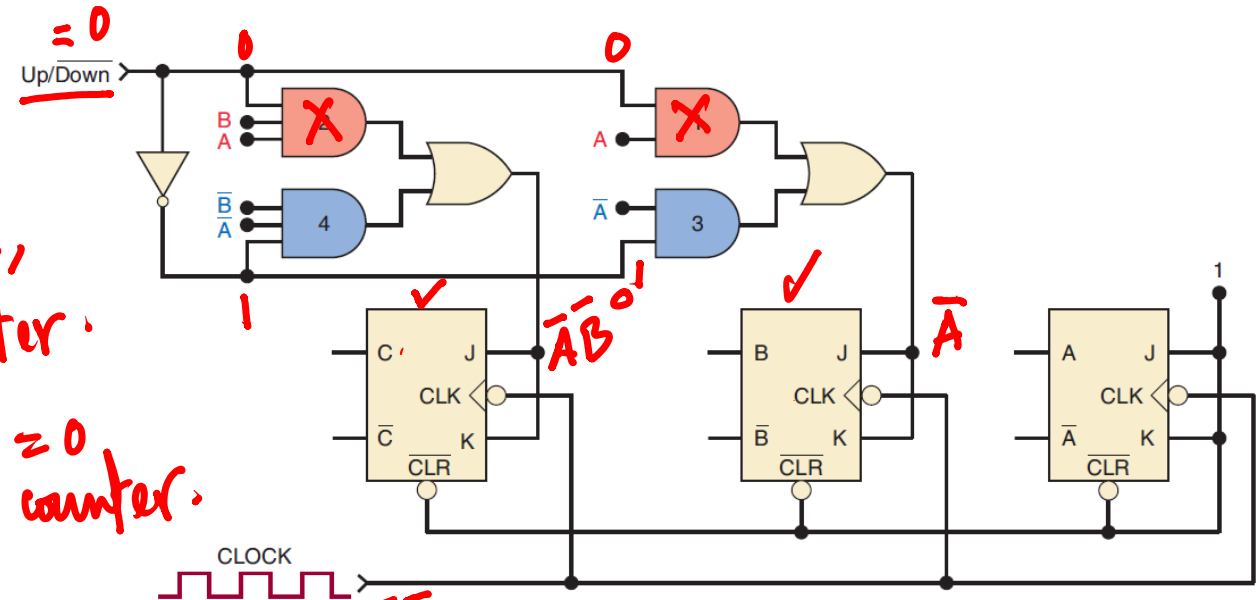

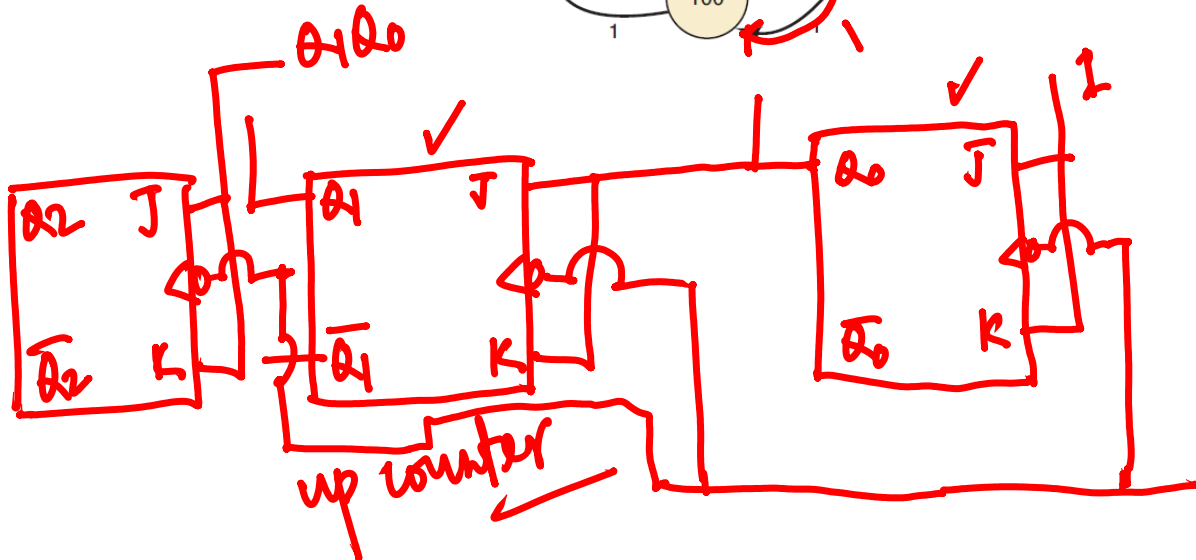up/down = 1,
up counter.
up/down = 0
down counter.



COUNTER CIRCUIT

0 → 600

- BCD counter: (up counter) (T flip-flop) · (4 bit)

T_{Q4} } → practice.

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	T_{Q8}	T_{Q4}	T_{Q2}	T_{Q1}
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$\checkmark T_{Q1} = 1$
 $\checkmark T_{Q2} = Q_8' Q_1$
 $T_{Q4} = Q_2 Q_1$
 $T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$
 $y = Q_8 Q_1$

T_{Q1} $Q_8 Q_1$

	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	X	X	X	X
10	1	1	X	X


$T_{Q1} = 1$

T_{Q2} $Q_2 Q_1$

	00	01	11	10
00		1	1	
01		1	1	
11	X	X	X	X
10			X	X

$T_{Q2} = \bar{Q}_8 Q_1$


T	Q
0	NC
1	Toggle

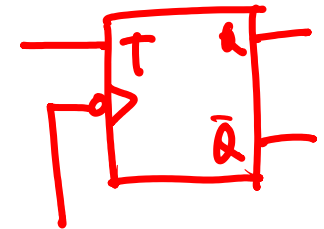

COUNTER CIRCUIT

- Synchronous counter with different control input:
- A circuit with n flip-flops has 2^n binary states. There are occasions when a sequential circuit uses fewer than this maximum possible number of states.
- States that are not used in specifying the sequential circuit are not listed in the state table.
- In simplifying the input equations, the unused states may be treated as don't-care conditions or may be assigned specific next states

PRESENT State			Control Inputs						NEXT State		
C	B	A	J_C	K_C	J_B	K_B	J_A	K_A	C	B	A
0	0	0	0	0	0	0	1	1	0	0	1
0	0	1	0	0	1	1	1	1	0	1	0
0	1	0	0	0	0	0	1	1	0	1	1
0	1	1	1	0	1	1	1	1	1	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	0	0	0	1	1
1	1	0	0	1	0	0	0	0	0	1	0
1	1	1	1	1	1	1	0	0	0	0	1

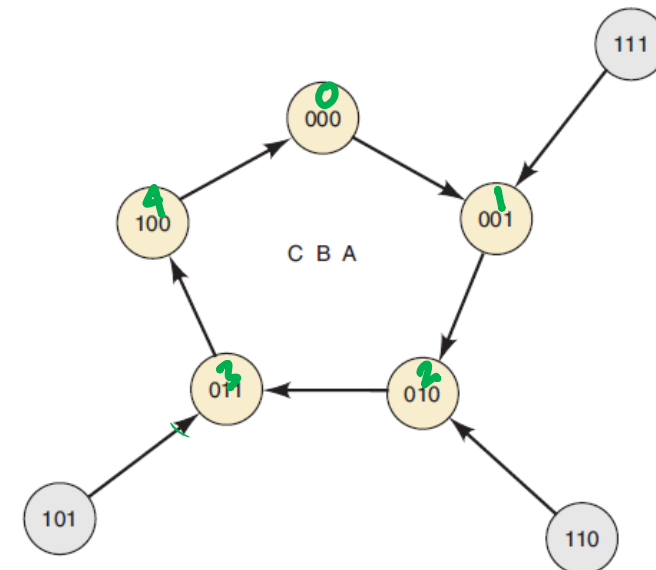


COUNTER CIRCUIT


- Synchronous counter with different control input:

PRESENT State			NEXT State			Control Inputs		
C	B	A	C	B	A	D_C	D_B	D_A
0→0	0	0	1→0	0	1	0	0	1✓
1→0	0	1	2→0	1	0	0	1	0
2→0	1	0	3→0	1	1	0	1	1
3→0	1	1	4→1	0	0	1	0	0
4→1	0	0	5→1	0	1	1	0	1
5→1	0	1	6→1	1	0	1	1	0
6→1	1	0	7→1	1	1	1	1	1
7→1	1	1	0→0	0	0	0	0	0


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

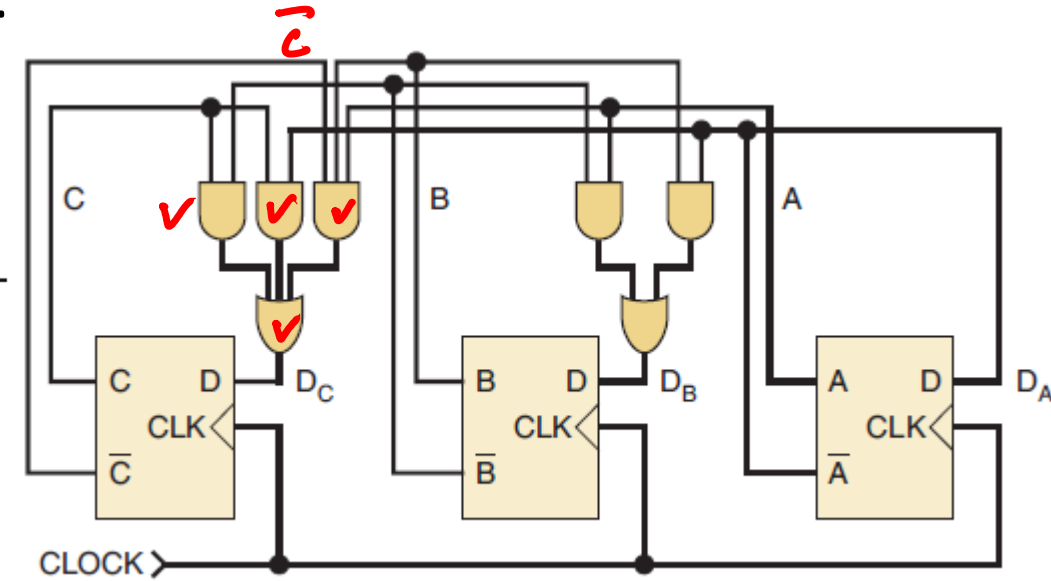

D_C

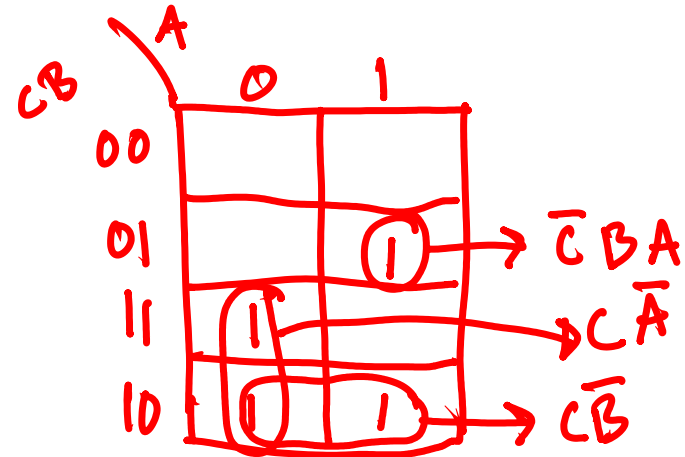
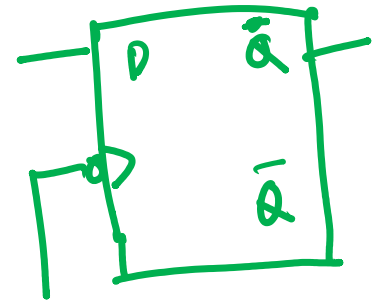
$$D_C = \bar{C}BA + C\bar{A} + C\bar{B}$$




COUNTER CIRCUIT

- Synchronous counter with different control input:
- Homework:

PRESENT State			NEXT State		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$T \rightarrow$

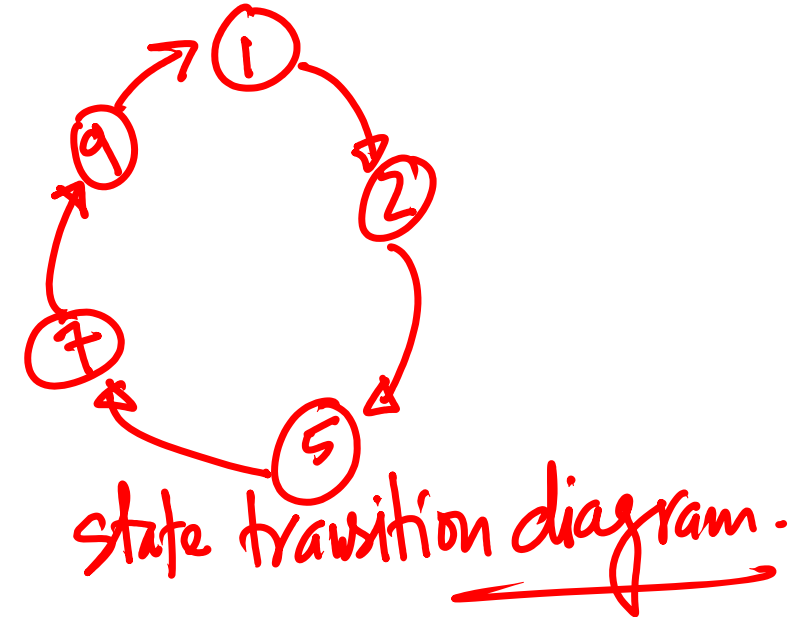



T Flip-Flop

T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement


COUNTER CIRCUIT

- Synchronous counter with different control input:
- J-K excitation Table:

Transition at FF Output	PRESENT State Q_n	NEXT State Q_{n+1}	J	K
0 → 0	0	0	0	x
0 → 1	0	1	1	x
1 → 0	1	0	x	1
1 → 1	1	1	x	0

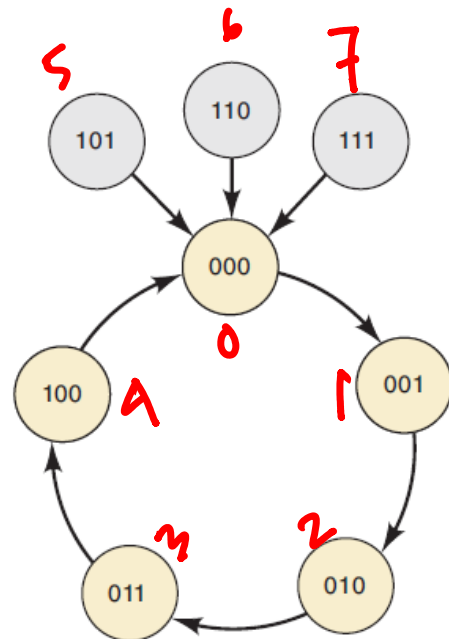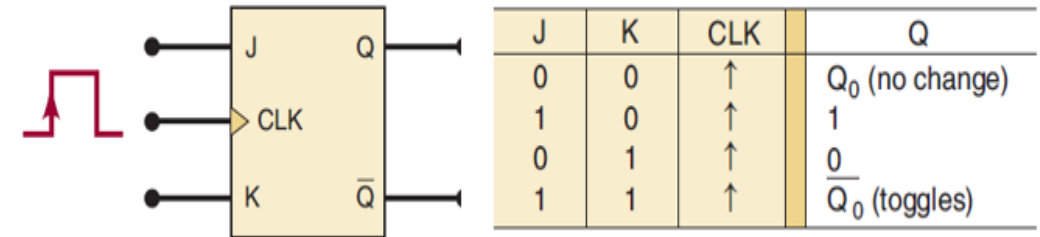


		PRESENT State			NEXT State								
		C	B	A	C	B	A	J_C	K_C	J_B	K_B	J_A	K_A
Line 1	0	0	0	0	0	0	1	0	x	0	x	1	x
2	1	0	0	1	0	1	0	0	x	1	x	x	1
3	2	0	1	0	0	1	1	0	x	x	0	1	x
4	3	0	1	1	1	0	0	1	x	x	1	x	1
5	4	1	0	0	0	0	0	x	1	0	x	0	x
6	5	1	0	1	0	0	0	x	1	0	x	x	1
7	6	1	1	0	0	0	0	x	1	x	1	0	x
8	7	1	1	1	0	0	0	x	1	x	1	x	1

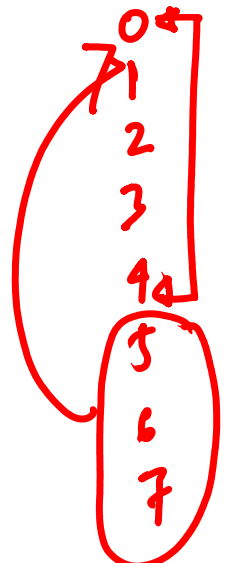

COUNTER CIRCUIT

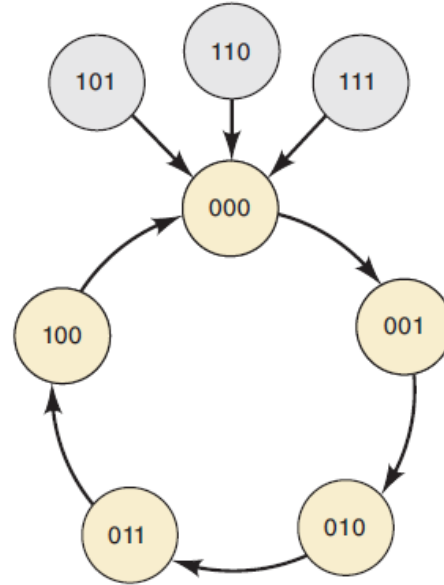- Synchronous counter with different control input:
- J-K excitation Table:




	PRESENT State			NEXT State			J_C	K_C	J_B	K_B	J_A	K_A
	C	B	A	C	B	A						
Line 1	0	0	0	0	0	1	0	x	0	x	1	x
2	0	0	1	0	1	0	0	x	1	x	x	1
3	0	1	0	0	1	1	0	x	x	0	1	x
4	0	1	1	1	0	0	1	x	x	1	x	1
5	1	0	0	0	0	0	x	1	0	x	0	x
6	1	0	1	0	0	0	x	1	0	x	x	1
7	1	1	0	0	0	0	x	1	x	1	0	x
8	1	1	1	0	0	0	x	1	x	1	x	1






COUNTER CIRCUIT

- Synchronous counter with different control input:

- J-K excitation Table:

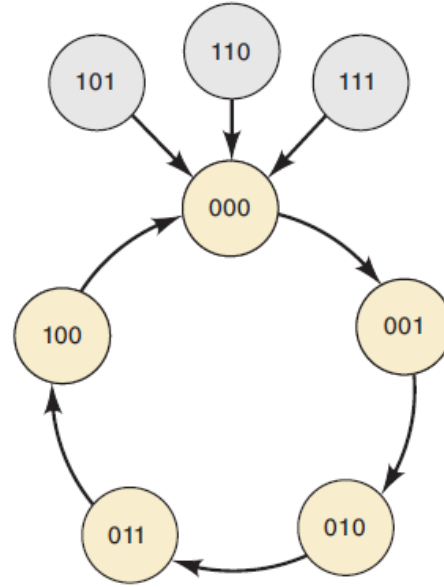


Line	PRESENT State			NEXT State			J_C	K_C	J_B	K_B	J_A	K_A
	C	B	A	C	B	A						
1	0	0	0	0	0	1	0	x	0	x	1	x
2	0	0	1	0	1	0	0	x	1	x	x	1
3	0	1	0	0	1	1	0	x	x	0	1	x
4	0	1	1	1	0	0	1	x	x	1	x	1
5	1	0	0	0	0	0	x	1	0	x	0	x
6	1	0	1	0	0	0	x	1	0	x	x	1
7	1	1	0	0	0	0	x	1	x	1	0	x
8	1	1	1	0	0	0	x	1	x	1	x	1

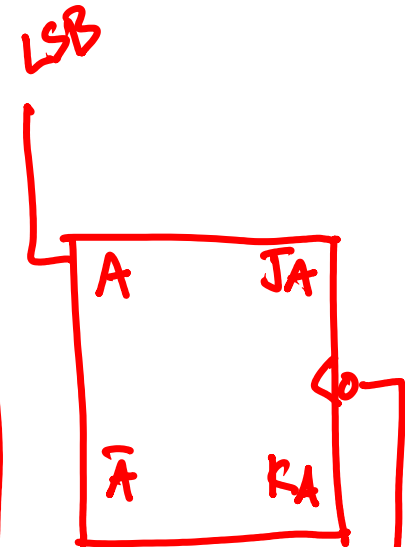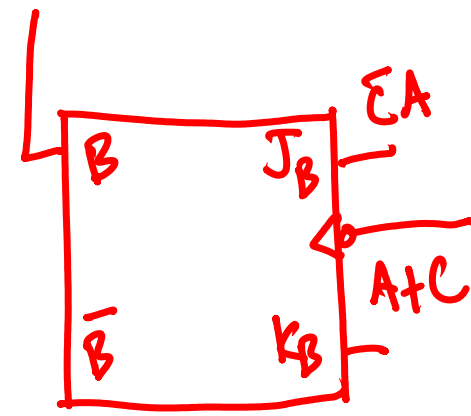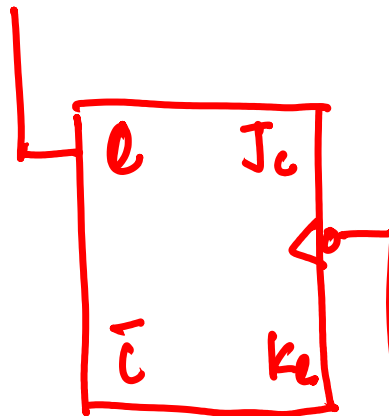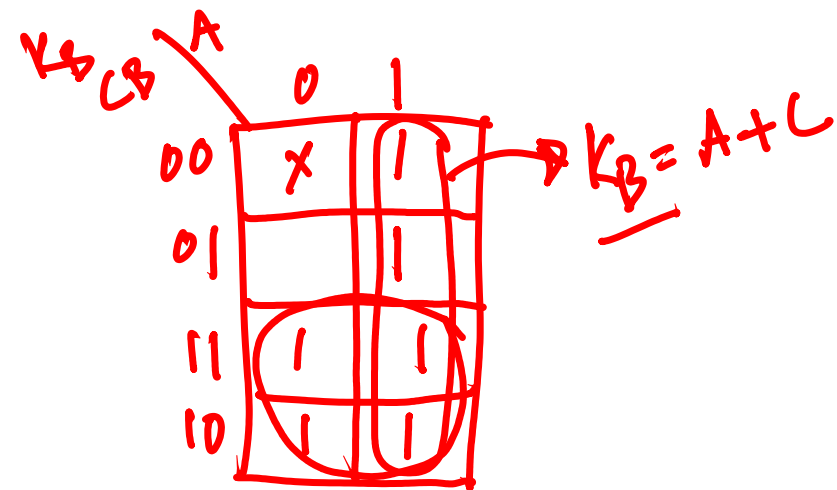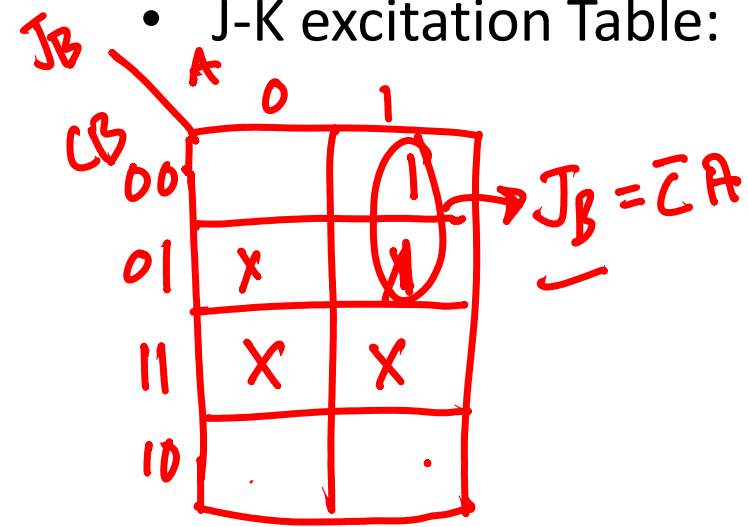

COUNTER CIRCUIT

Y contr of command.

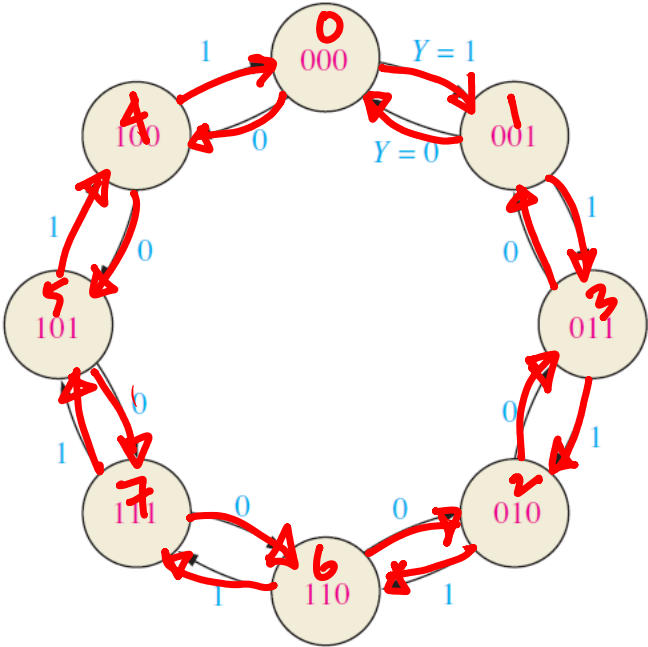Develop a synchronous 3-bit up/down counter with a Gray code sequence using J-K flip-flops. The counter should count up when an $\overline{\text{UP/DOWN}}$ control input is 1 and count down when the control input is 0.



Next-state table for 3-bit up/down Gray code counter.


Present State			Next State					
			Y = 0 (DOWN)			Y = 1 (UP)		
Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀
0 → 0	0	0	4 → 1	0	0	1 → 0	0	1
1 → 0	0	1	0 → 0	0	0	3 → 0	1	1
2 → 0	1	1	1 → 0	0	1	2 → 0	1	0
3 → 0	1	0	3 → 0	1	1	6 → 1	1	0
6 → 1	1	0	2 → 0	1	0	7 → 1	1	1
7 → 1	1	1	6 → 1	1	0	5 → 1	0	1
4 → 1	0	1	1 → 1	1	1	4 → 1	0	0
5 → 1	0	0	5 → 1	0	1	0 → 0	0	0

Y = $\overline{\text{UP/DOWN}}$ control input.

COUNTER CIRCUIT

Develop a synchronous 3-bit up/down counter with a Gray code sequence using J-K flip-flops. The counter should count up when an $\overline{\text{UP/DOWN}}$ control input is 1 and count down when the control input is 0.

Transition at FF Output	PRESENT State Q_n	NEXT State Q_{n+1}	J	K
0 → 0	0	0	0	x
0 → 1	0	1	1	x
1 → 0	1	0	x	1
1 → 1	1	1	x	0

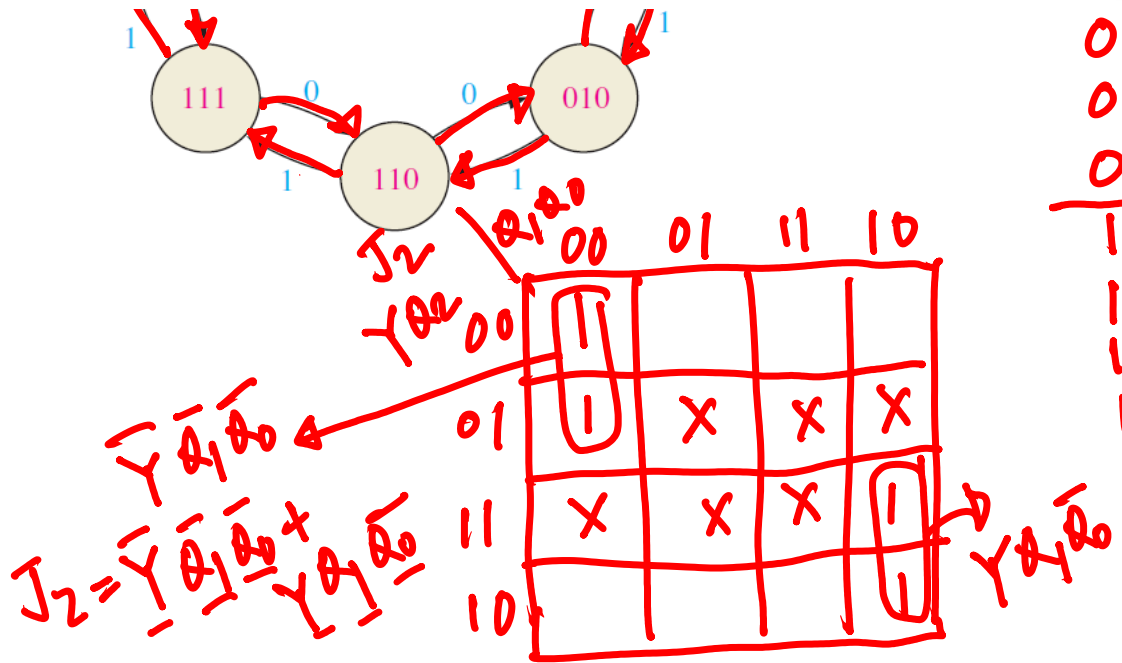

PRESENT	next stage	J ₂ K ₂	J ₁ K ₁	J ₀ K ₀
$Q_2 Q_1 Q_0$	$Q_2^+ Q_1^+ Q_0^+$			
0 0 0	1 0 0	1 x		
0 0 1	0 0 0	0 x		
0 1 0	0 1 1	0 x		
0 1 1	0 0 1	0 x		
1 0 0	1 0 1	x 0		
1 0 1	1 1 1	x 0		
1 1 0	1 1 0	x 1		
1 1 1	1 1 0	x 0		
0 0 0	1 0 0	0 x		
0 0 1	0 0 0	0 x		
0 1 0	0 1 1	1 x		
0 1 1	0 0 1	0 x		
1 0 0	1 0 1	x 1		
1 0 1	1 1 1	x 0		
1 1 0	1 1 0	x 0		
1 1 1	1 1 0	x 0		

COUNTER CIRCUIT

Develop a synchronous 3-bit up/down counter with a Gray code sequence using J-K flip-flops. The counter should count up when an $\overline{\text{UP/DOWN}}$ control input is 1 and count down when the control input is 0.

Next-state table for 3-bit up/down Gray code counter.

Present State			Next State					
			Y = 0 (DOWN)			Y = 1 (UP)		
			Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0

Y = UP/ $\overline{\text{DOWN}}$ control input.

$$J_0 = Q_2Q_1Y + Q_2\overline{Q_1}\overline{Y} + \overline{Q_2}\overline{Q_1}Y + \overline{Q_2}Q_1\overline{Y}$$
$$J_1 = \overline{Q_2}Q_0Y + Q_2Q_0\overline{Y}$$
$$J_2 = \underline{Q_1\overline{Q_0}Y} + \underline{\overline{Q_1}\overline{Q_0}\overline{Y}}$$

$$K_0 = \overline{Q_2}\overline{Q_1}\overline{Y} + \overline{Q_2}Q_1Y + Q_2\overline{Q_1}Y + Q_2Q_1\overline{Y}$$
$$K_1 = \overline{Q_2}Q_0\overline{Y} + Q_2Q_0Y$$
$$K_2 = Q_1\overline{Q_0}\overline{Y} + \overline{Q_1}\overline{Q_0}Y$$

	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀