
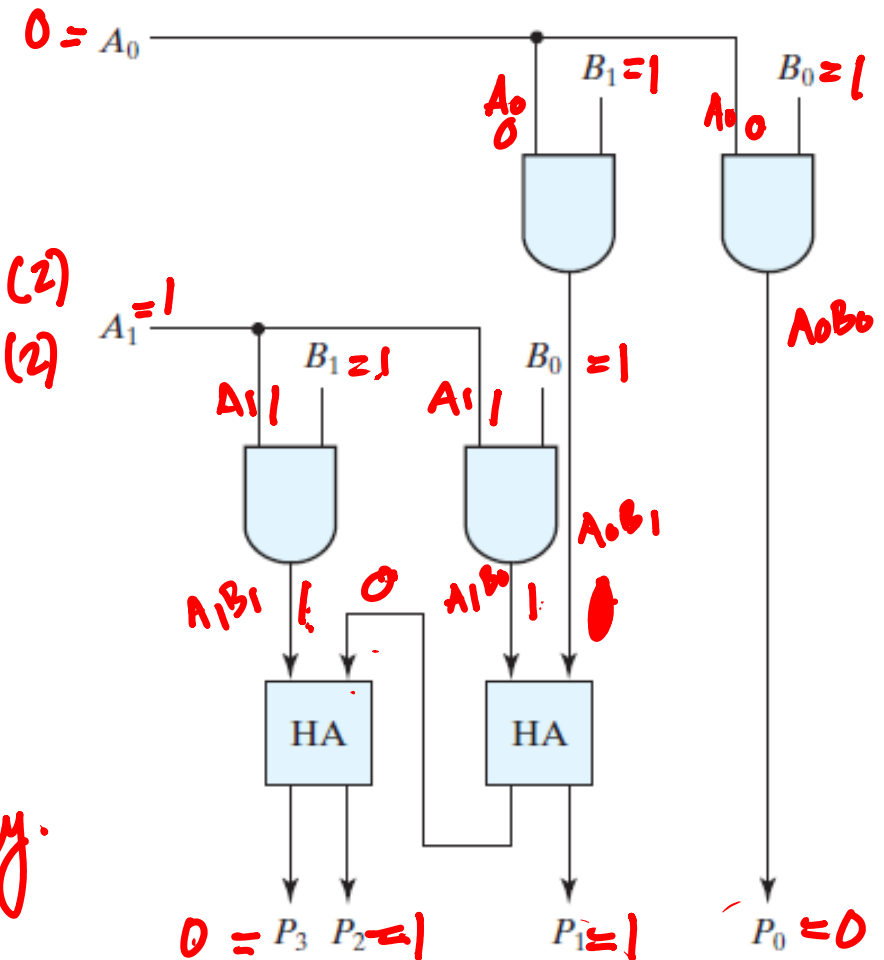
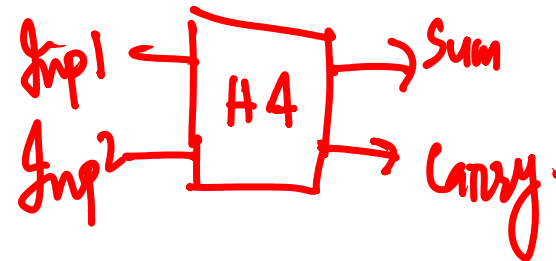
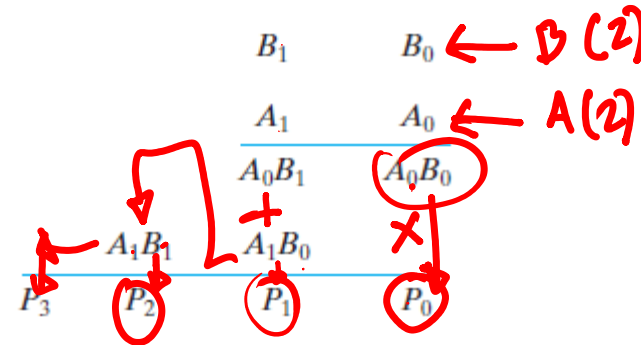



MULTIPLIER CIRCUIT

- Two bit by two bit multiplier:

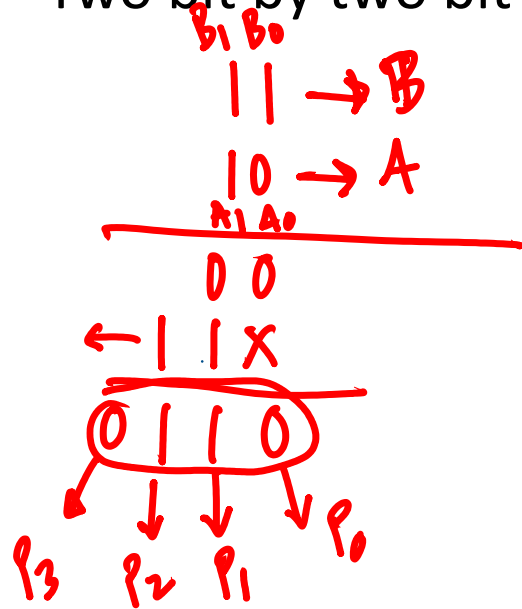

MULTIPLIER CIRCUIT

- Four-bit by three-bit multiplier:

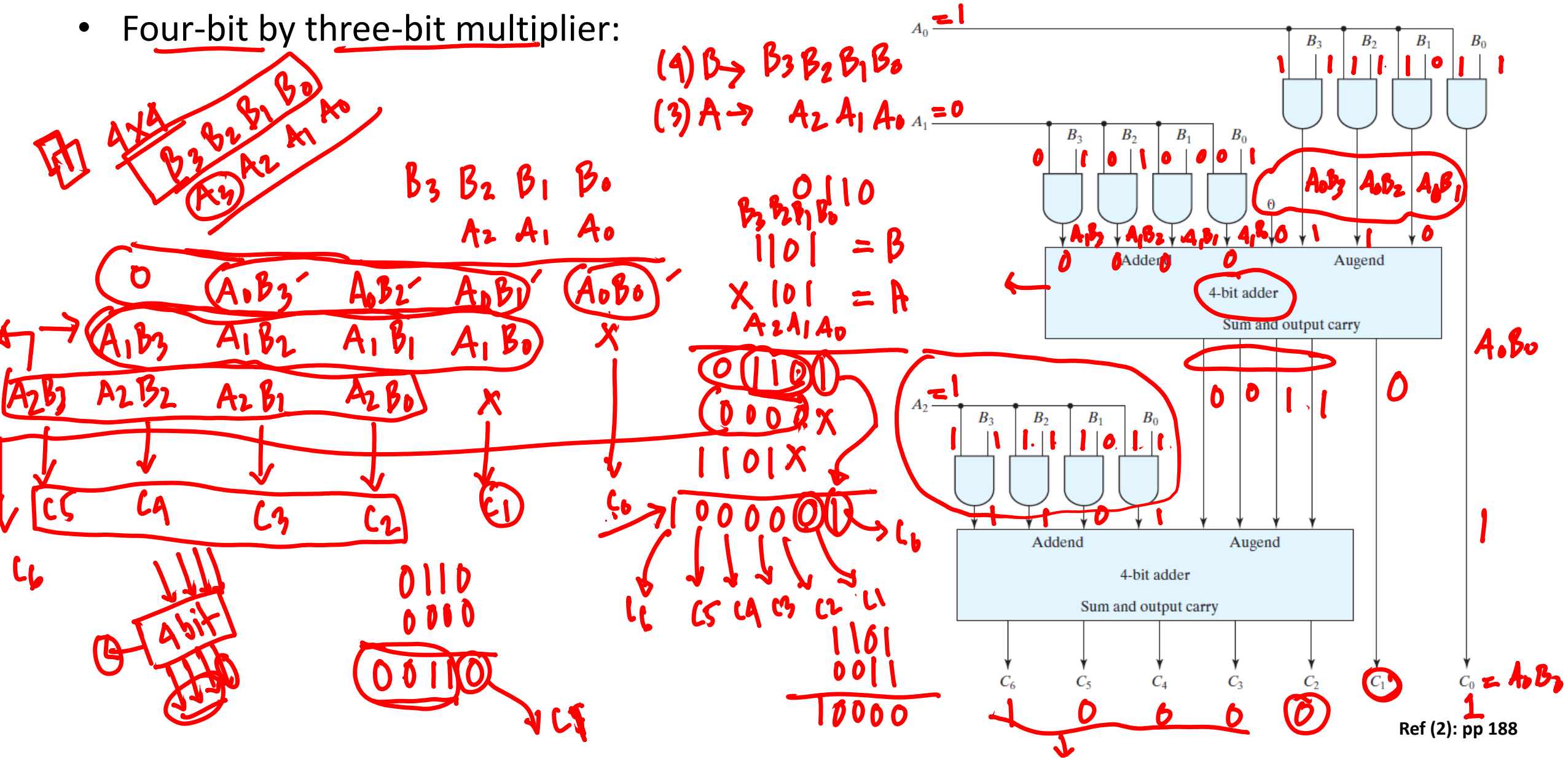


➔ MULTIPLEXER (Data selector).

- Two to one line multiplexer:

Multiplexer

→ So many inputs.
→ only one output.


$$2^1 = 2$$

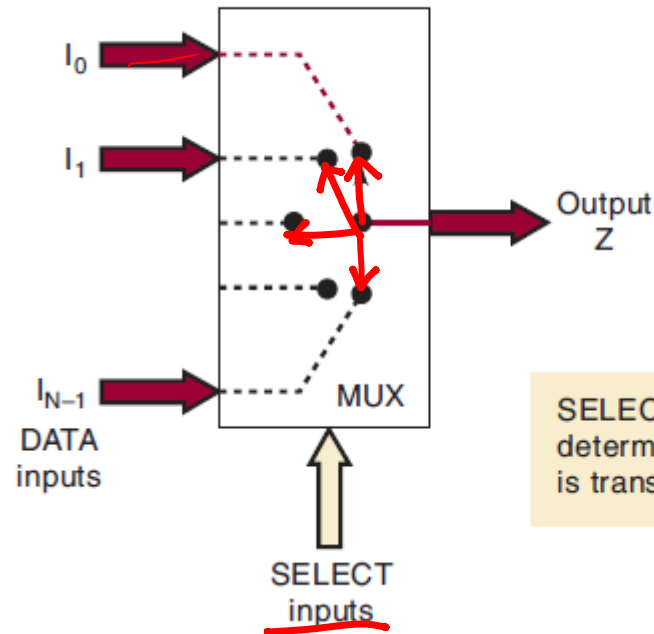



SELECT input code determines which input is transmitted to output Z .

S	Z
0	I_0
1	I_1

$$Z = \bar{S} I_0 + S I_1$$

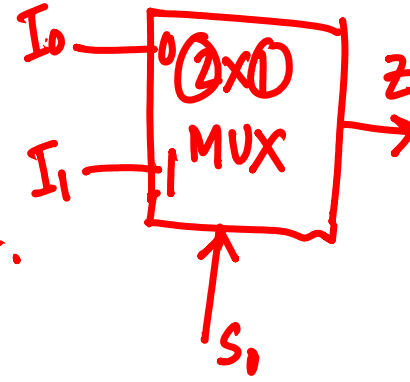


Block diagram

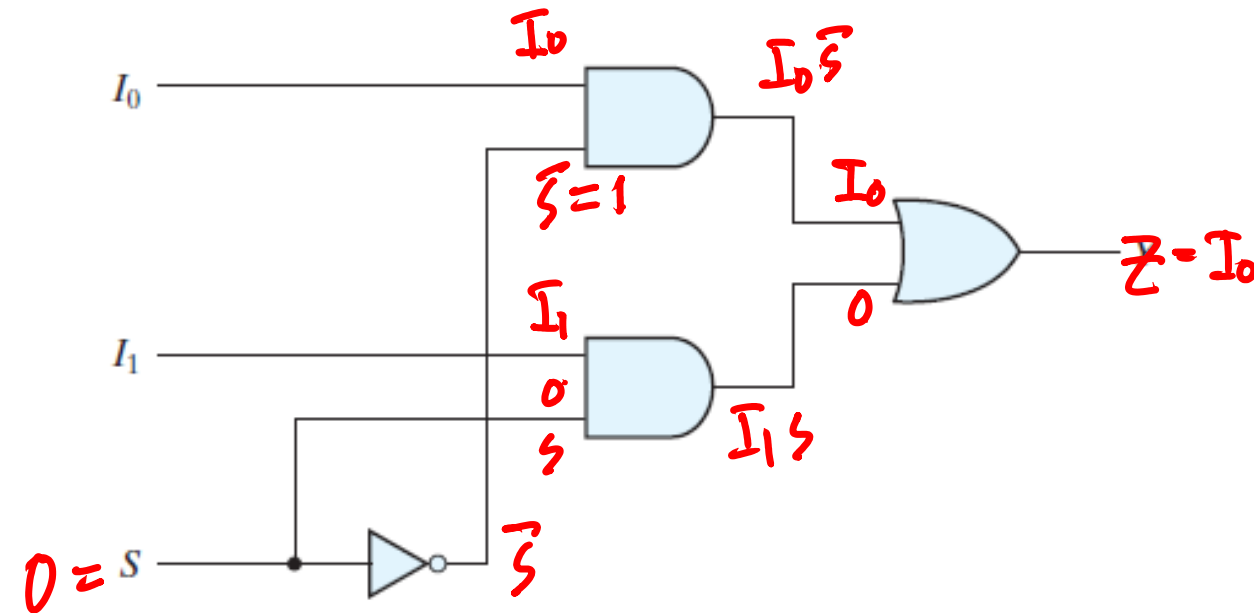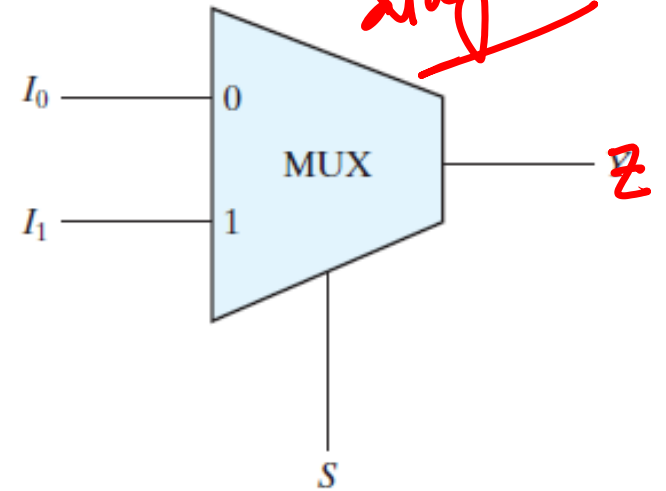

MULTIPLEXER

- Four to one line multiplexer:

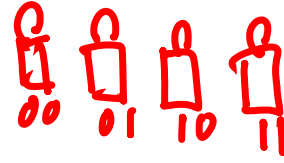


$$2^2 = 4$$




s_1	s_0	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
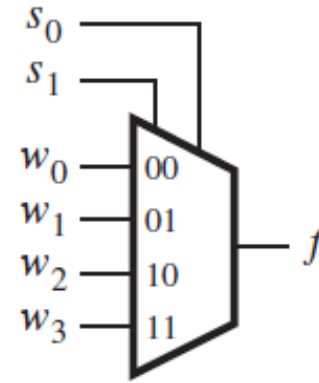
$$Z = \bar{s}_1 \bar{s}_0 I_0 + \bar{s}_1 s_0 I_1 + s_1 \bar{s}_0 I_2 + s_1 s_0 I_3$$



s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

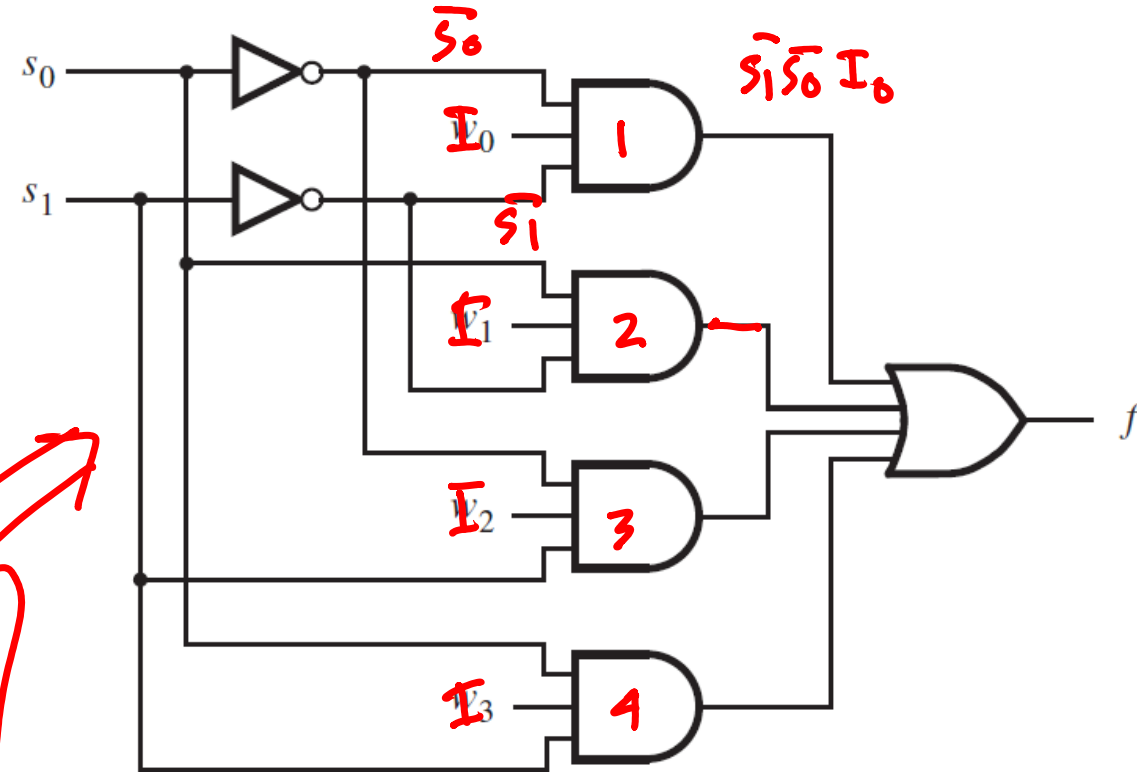


MULTIPLEXER

- Four to one line multiplexer by two to one line multiplexer :

$$\frac{4}{2} = 2$$

$$\frac{2}{2} = 1$$

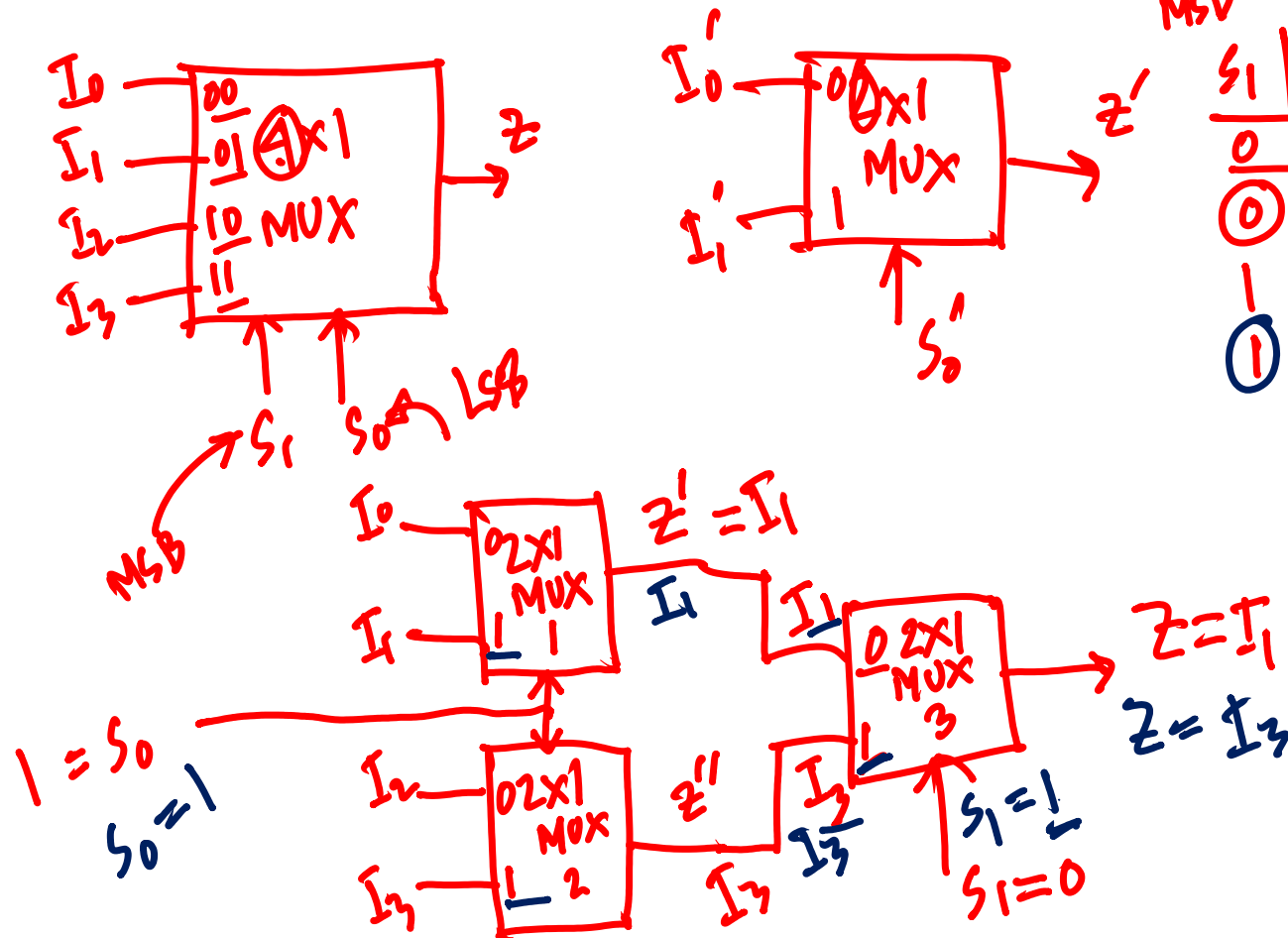

MSB	LSB	
s_1	s_0	z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

