
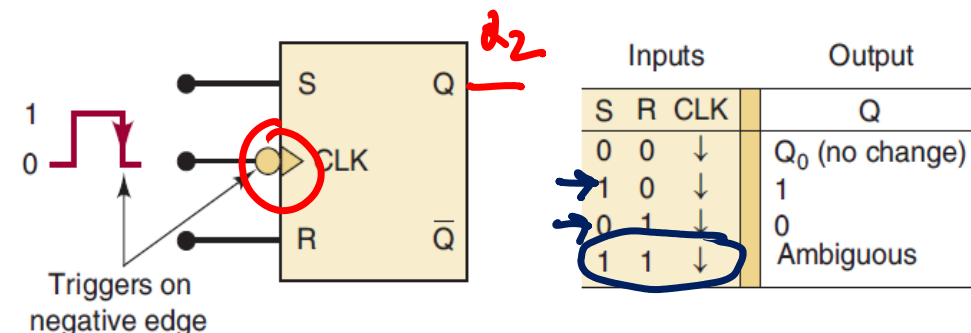
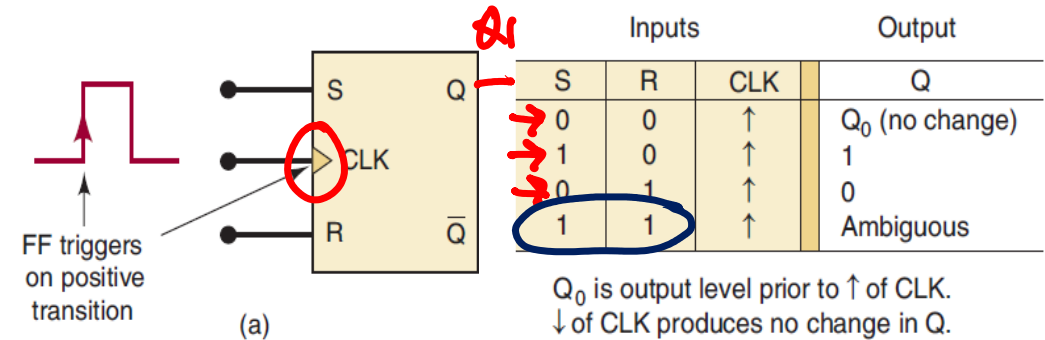


FLIP-FLOPS




- SR Flip-flop:

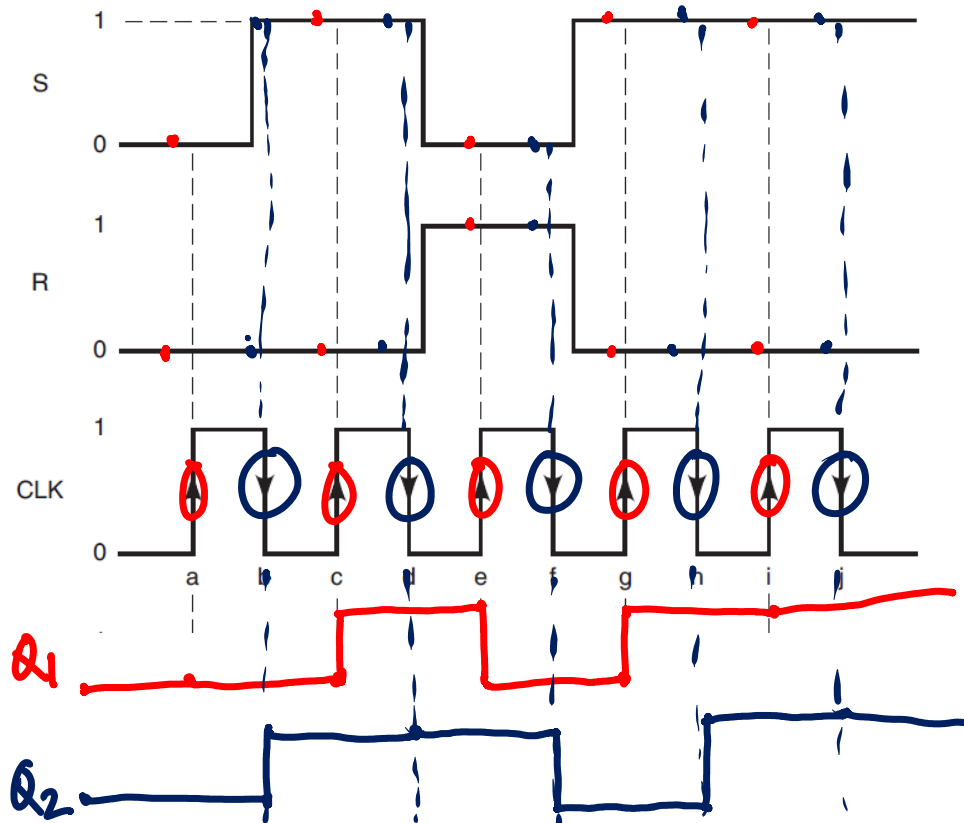A flip-flop is a storage element that can have its output state changed only on the edge of the controlling clock signal. If the state changes when the clock signal goes from 0 to 1, then the flip-flop is positive-edge triggered. If the state changes when the clock signal goes from 1 to 0, then the flip-flop is negative-edge triggered.



FLIP-FLOPS

- Clocked JK Flip-flop:

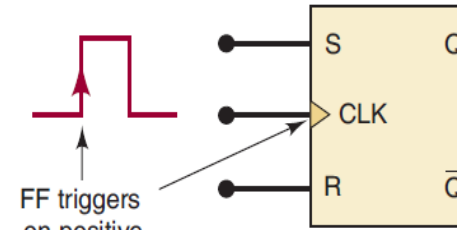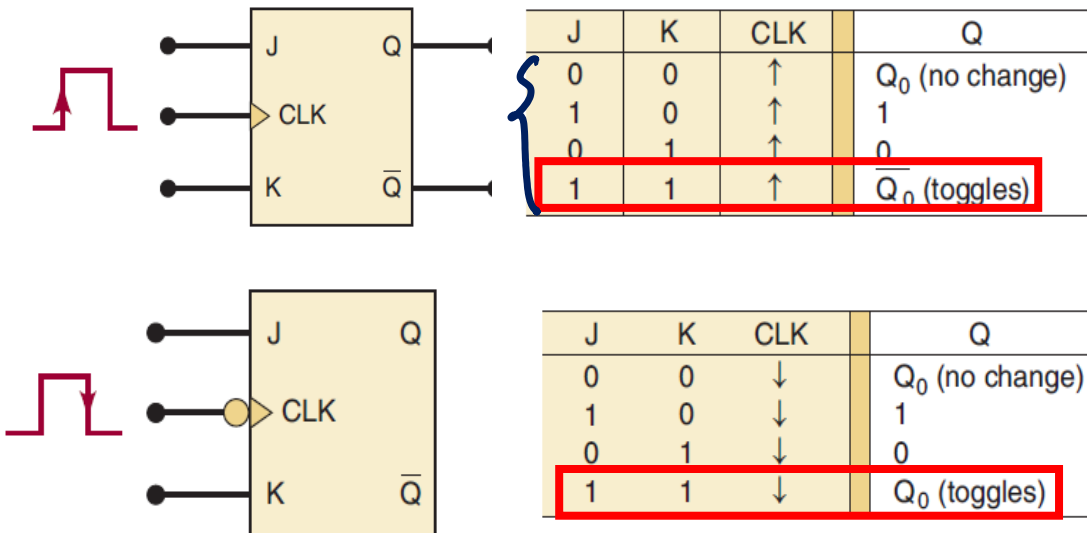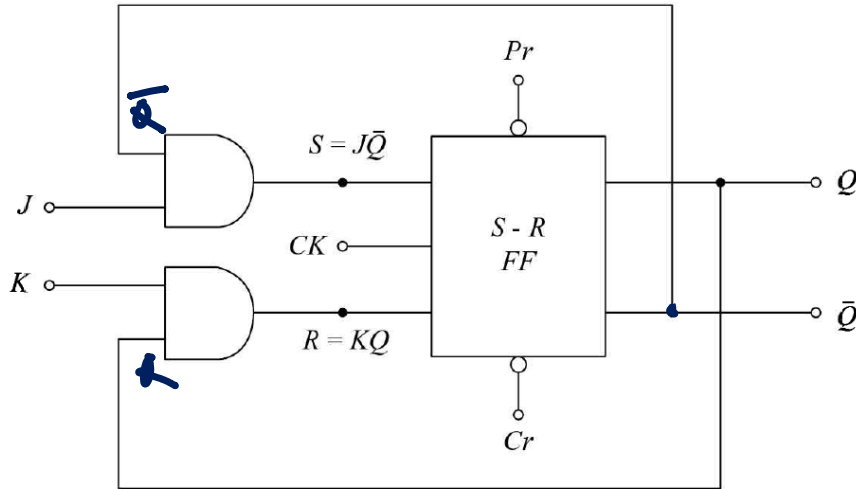

| Inputs | | | Output |
|--------|---|-----|-------------------|
| S | R | CLK | Q |
| 0 | 0 | ↑ | Q_0 (no change) |
| 1 | 0 | ↑ | 1 |
| 0 | 1 | ↑ | 0 |
| 1 | 1 | ↑ | Ambiguous |

Q_0 is output level prior to ↑ of CLK.
↓ of CLK produces no change in Q.


| J_n | K_n | Q_{n-1} | \overline{Q}_{n-1} | S_n | R_n | Q_n |
|-------|-------|-----------|----------------------|-------|-------|-------|
| 0 | 0 | →0 | 1 | 0 | 0 | →0 |
| 0 | 0 | →1 | 0 | 0 | 0 | →1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0→ | 1 | 1 | 0 | 1 |
| 1 | 1 | 1→ | 0 | 0 | 1 | 0 |

Handwritten notes on the right side of the table:

- $Q_n = Q_{n-1}$ for $J=0, K=0$
- $Q_n = 1$ for $J=1, K=0$
- $Q_n = 0$ for $J=0, K=1$
- $Q_n = \overline{Q_{n-1}}$ for $J=1, K=1$



FLIP-FLOPS

- Clocked JK Flip-flop:

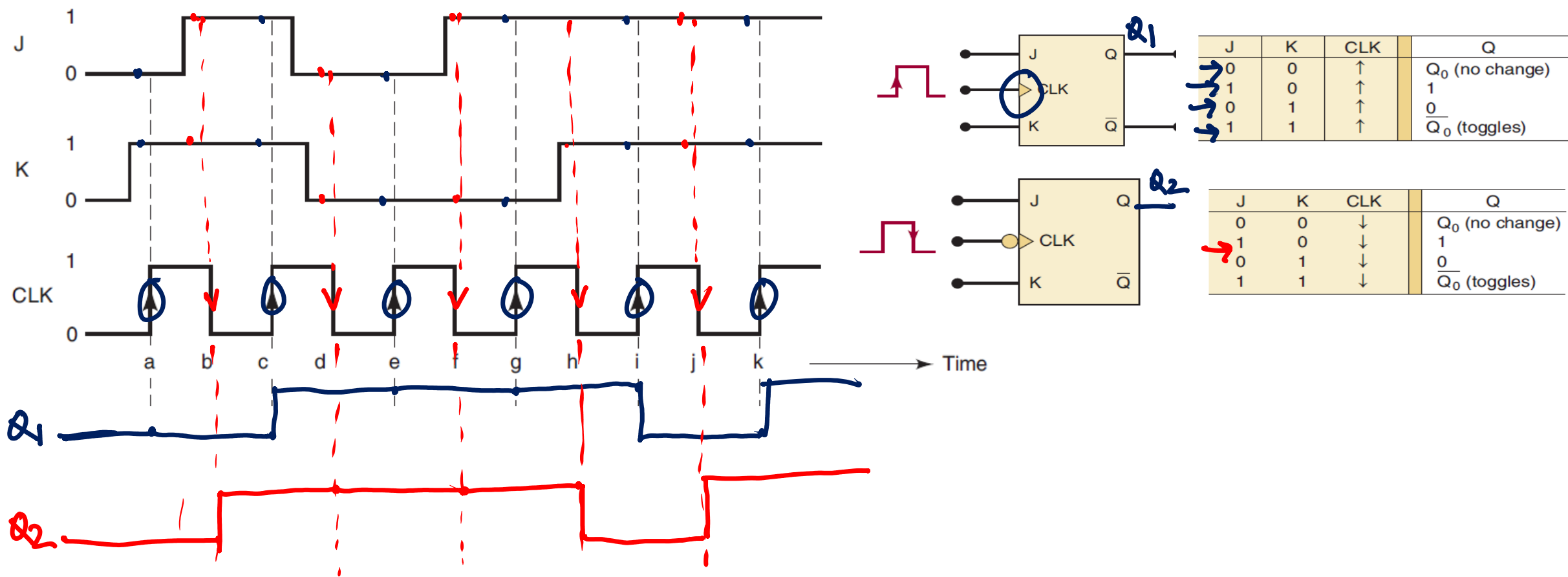

FLIP-FLOPS

- Clocked JK Flip-flop:

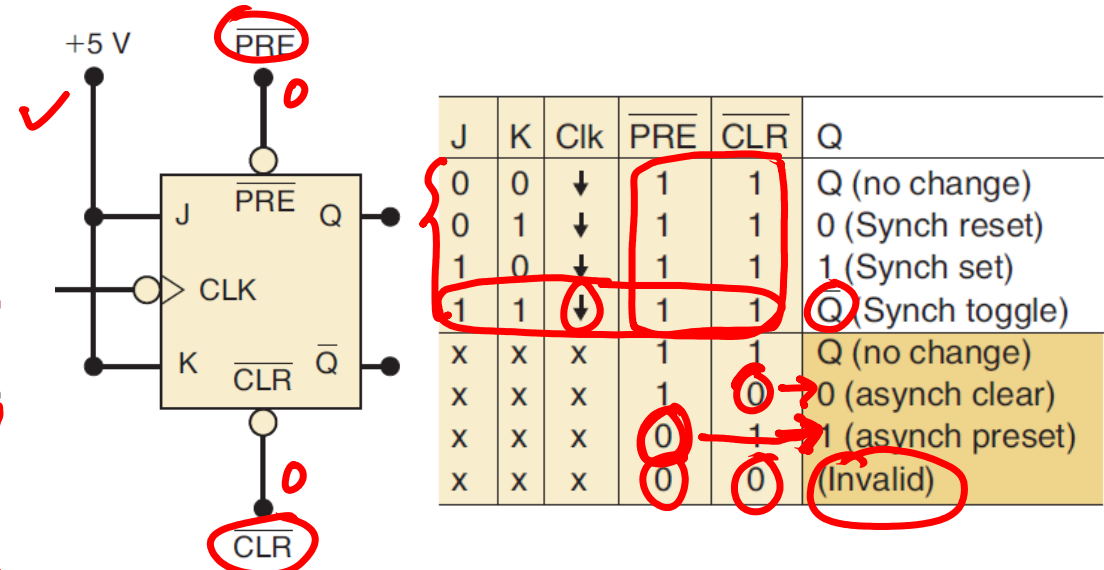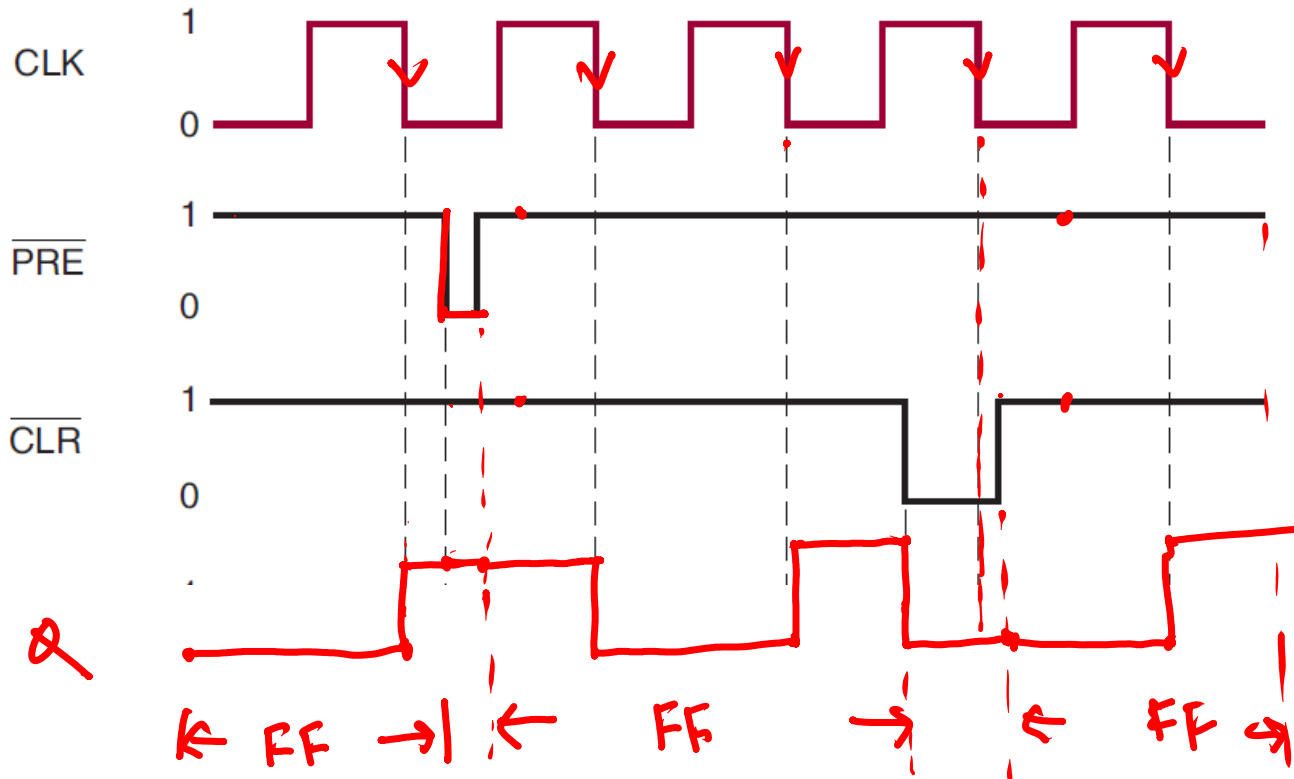


| J | K | Clk | $\overline{\text{PRE}}$ | $\overline{\text{CLR}}$ | Q |
|---|---|-----|-------------------------|-------------------------|--------------------------|
| 0 | 0 | ↓ | 1 | 1 | Q (no change) |
| 0 | 1 | ↓ | 1 | 1 | 0 (Synch reset) |
| 1 | 0 | ↓ | 1 | 1 | 1 (Synch set) |
| 1 | 1 | ↓ | 1 | 1 | \bar{Q} (Synch toggle) |
| x | x | x | 1 | 1 | Q (no change) |
| x | x | x | 1 | 0 | 0 (asynch clear) |
| x | x | x | 0 | 1 | 1 (asynch preset) |
| x | x | x | 0 | 0 | (Invalid) |


$\overline{\text{PRE}} = 1, \overline{\text{CLR}} = 1, \text{FF} \rightarrow \text{No operation}$

$J = K = +5V = 1$

FLIP-FLOPS

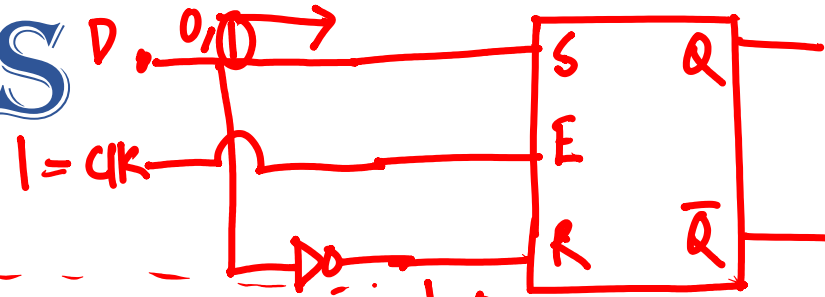

- D Latch:

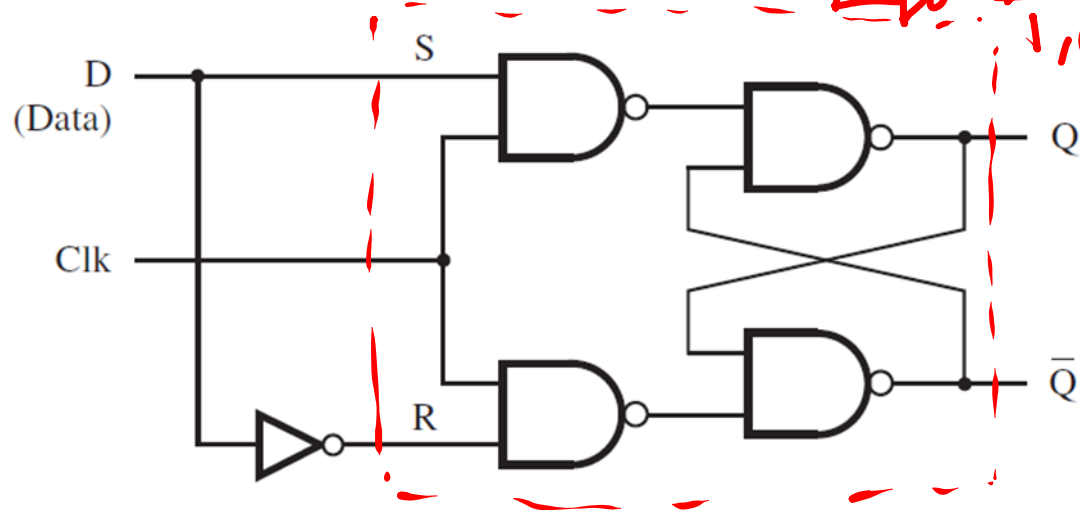



| En | S | R | Next state of Q |
|-----|---|---|-----------------------|
| → 0 | X | X | No change |
| → 1 | 0 | 0 | No change |
| → 1 | 0 | 1 | $Q = 0$; reset state |
| → 1 | 1 | 0 | $Q = 1$; set state |
| 1 | 1 | 1 | Indeterminate |

| Clk | D | $Q(t + 1)$ |
|-----|---|-------------|
| → 0 | x | $Q(t)$ (NC) |
| → 1 | 0 | 0 |
| → 1 | 1 | 1 |


| D | $S=D$ | $R=\bar{D}$ | Q |
|---|-------|-------------|-------------------|
| 0 | 0 | 1 | $\underline{Q=0}$ |
| 1 | 1 | 0 | $\underline{Q=1}$ |

FLIP-FLOPS

- Clocked D Flip-flop:

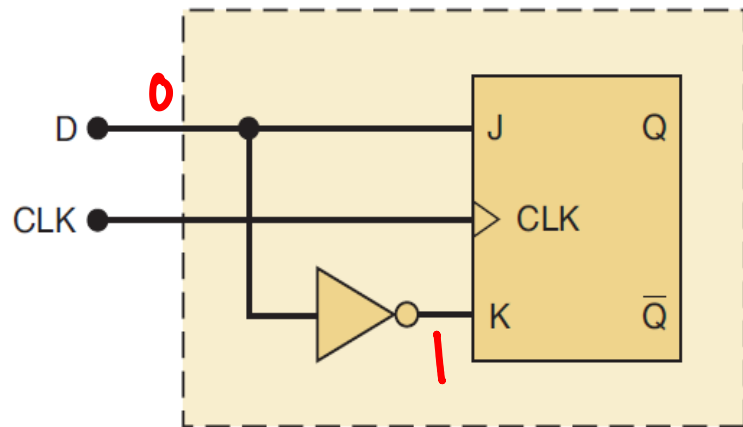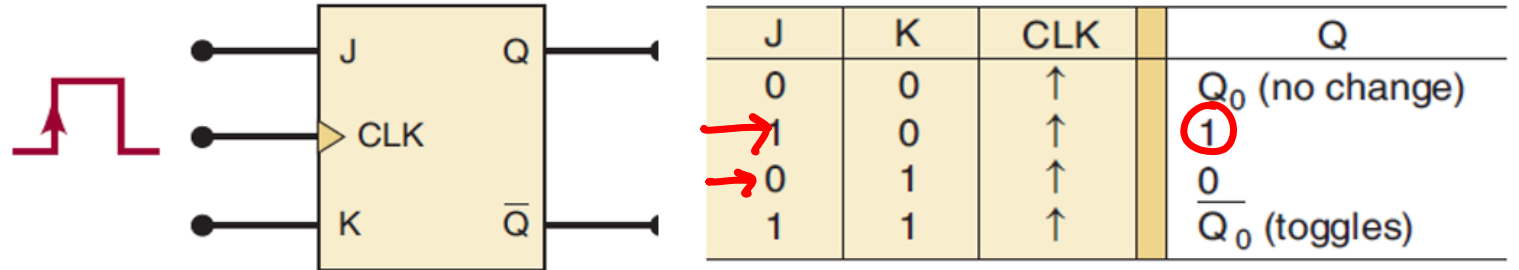


≡

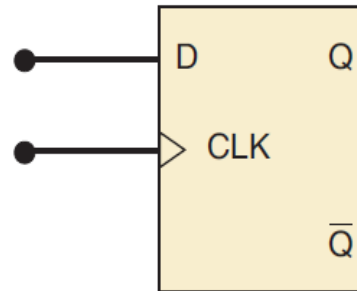



| D | J=D | K=D̄ | Q |
|---|-----|------|---|
| 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

FLIP-FLOPS

- Clocked D Flip-flop:

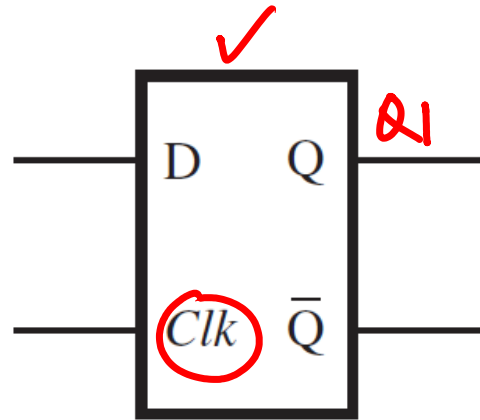


| Clk | D | $Q(t + 1)$ |
|-----|---|------------|
| → 0 | x | $Q(t)$ |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

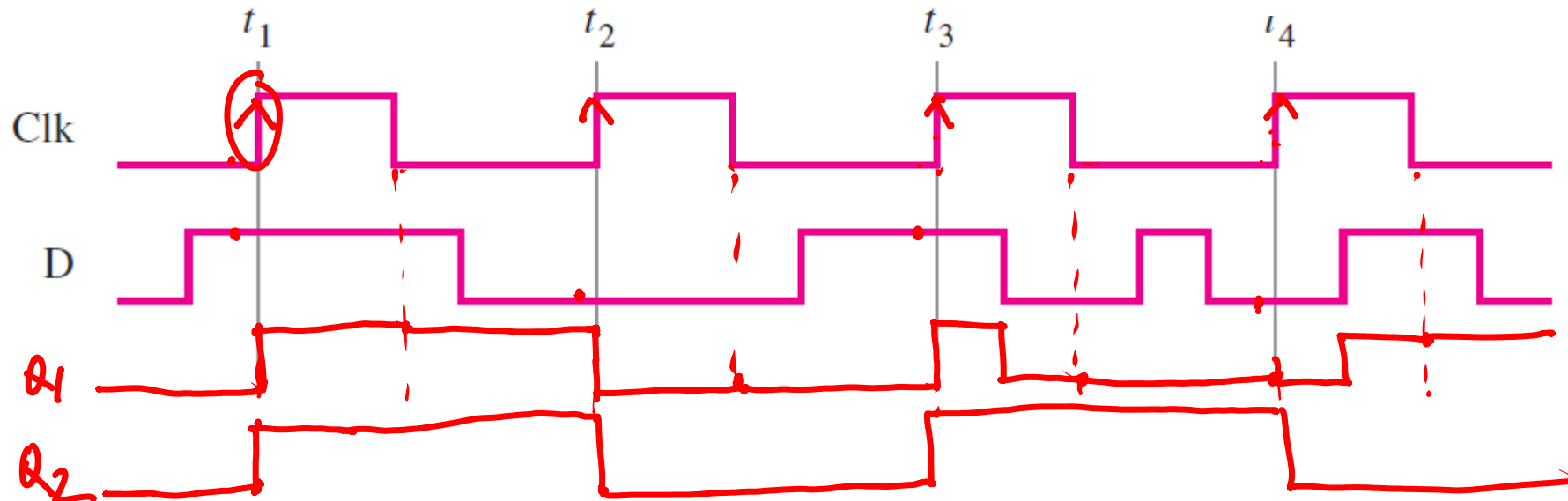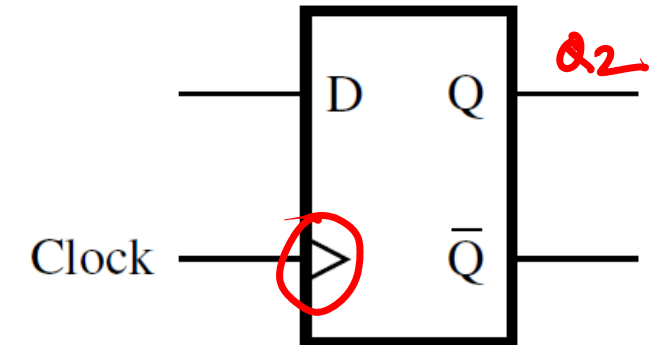

FLIP-FLOPS

- Clocked D Latch:

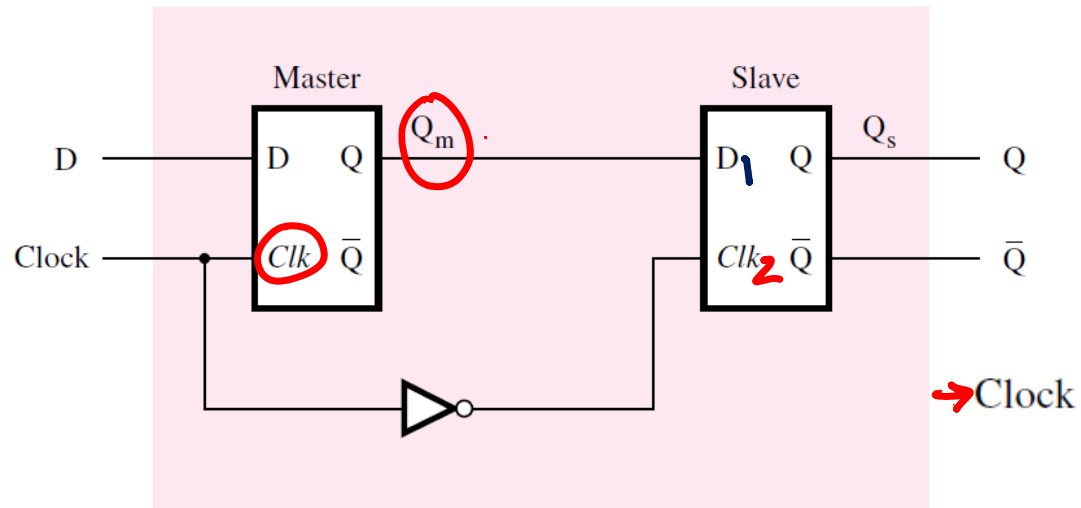

| Clk | D | Q(t + 1) |
|-----|---|----------|
| 0 | x | Q(t) |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

