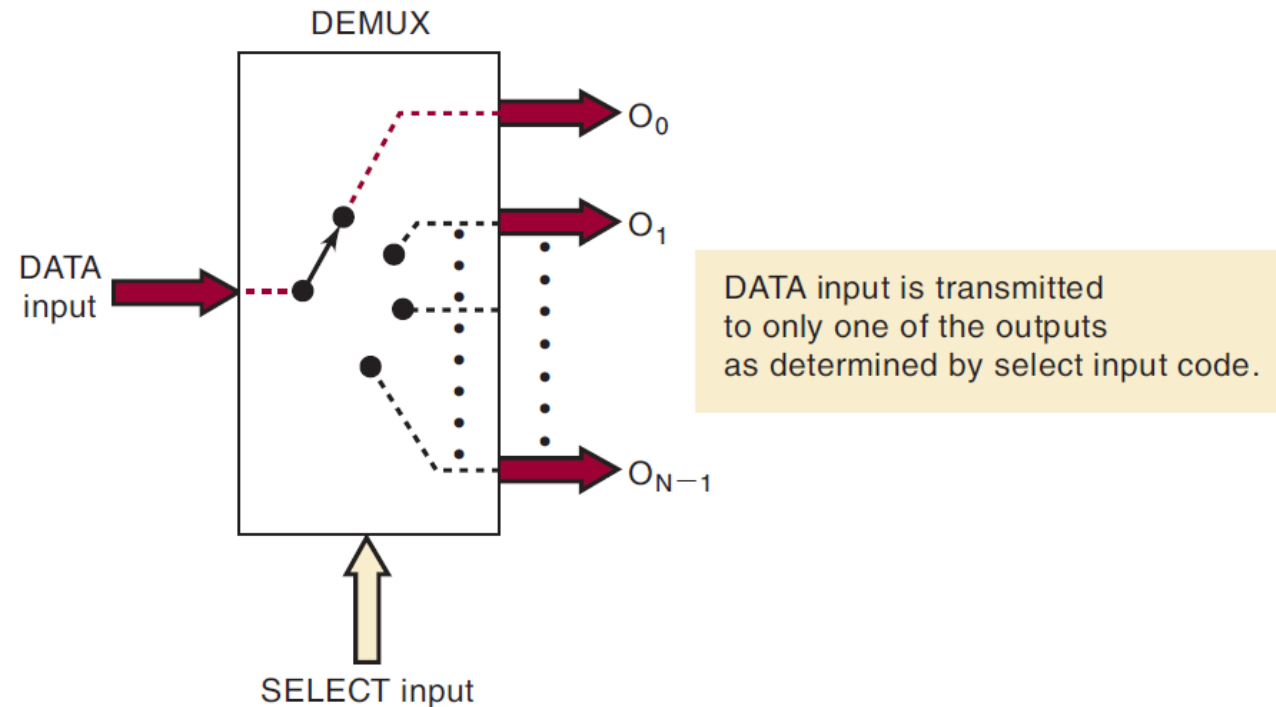


DEMULTIPLEXER CIRCUIT



- A demultiplexer circuit performs the opposite operations of multiplexer circuit.
- It takes one input and distributes it over several outputs.



DEMULTIPLEXER CIRCUIT



- 1-Line-to-8-Line Demultiplexer:

Select Code			Outputs							
S ₂	S ₁	S ₀	O ₇	O ₆	O ₅	O ₄	O ₃	O ₂	O ₁	O ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

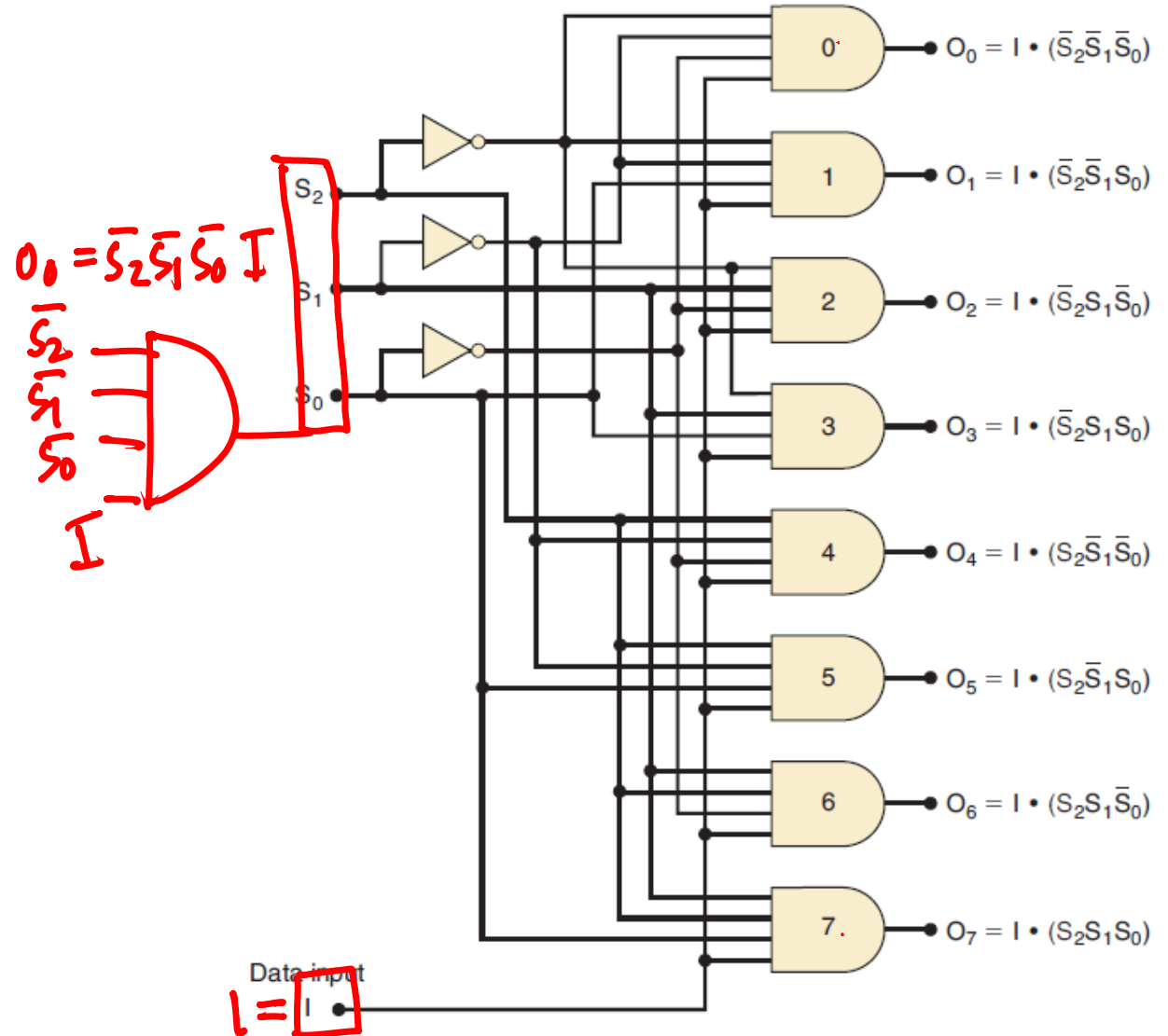
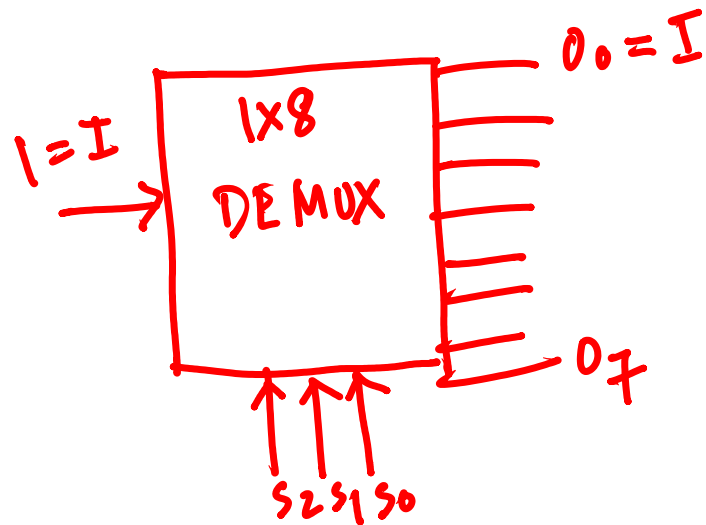


DEMULTIPLEXER CIRCUIT

- 1-Line-to-8-Line Demultiplexer:

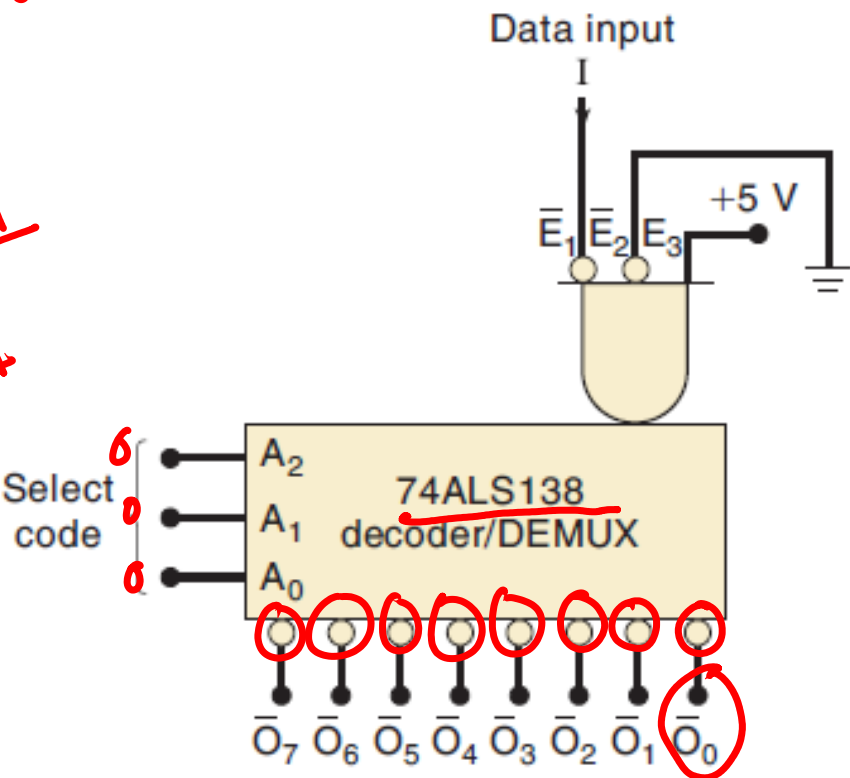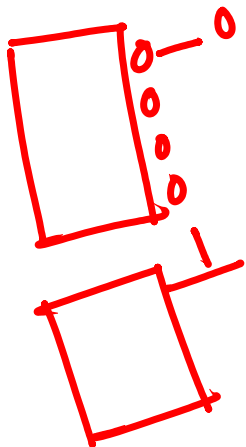


(a)

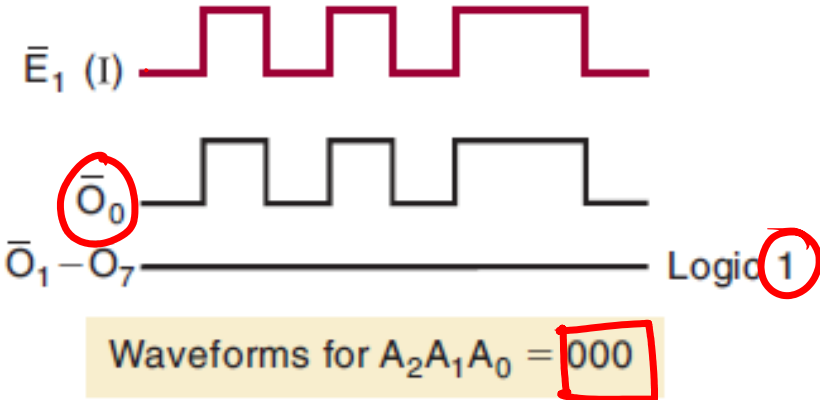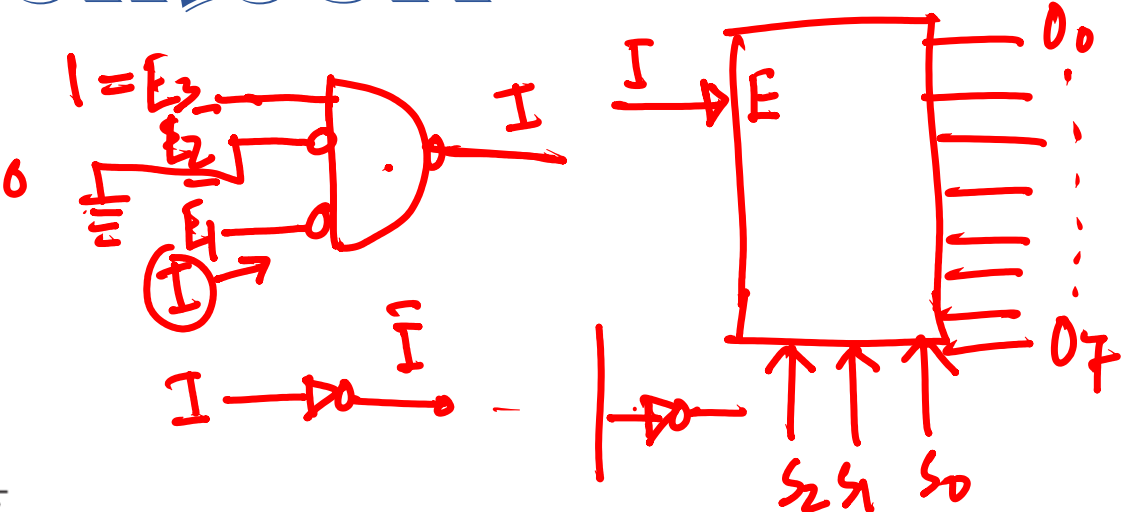

(b)

DEMULTIPLEXER CIRCUIT


- Application:

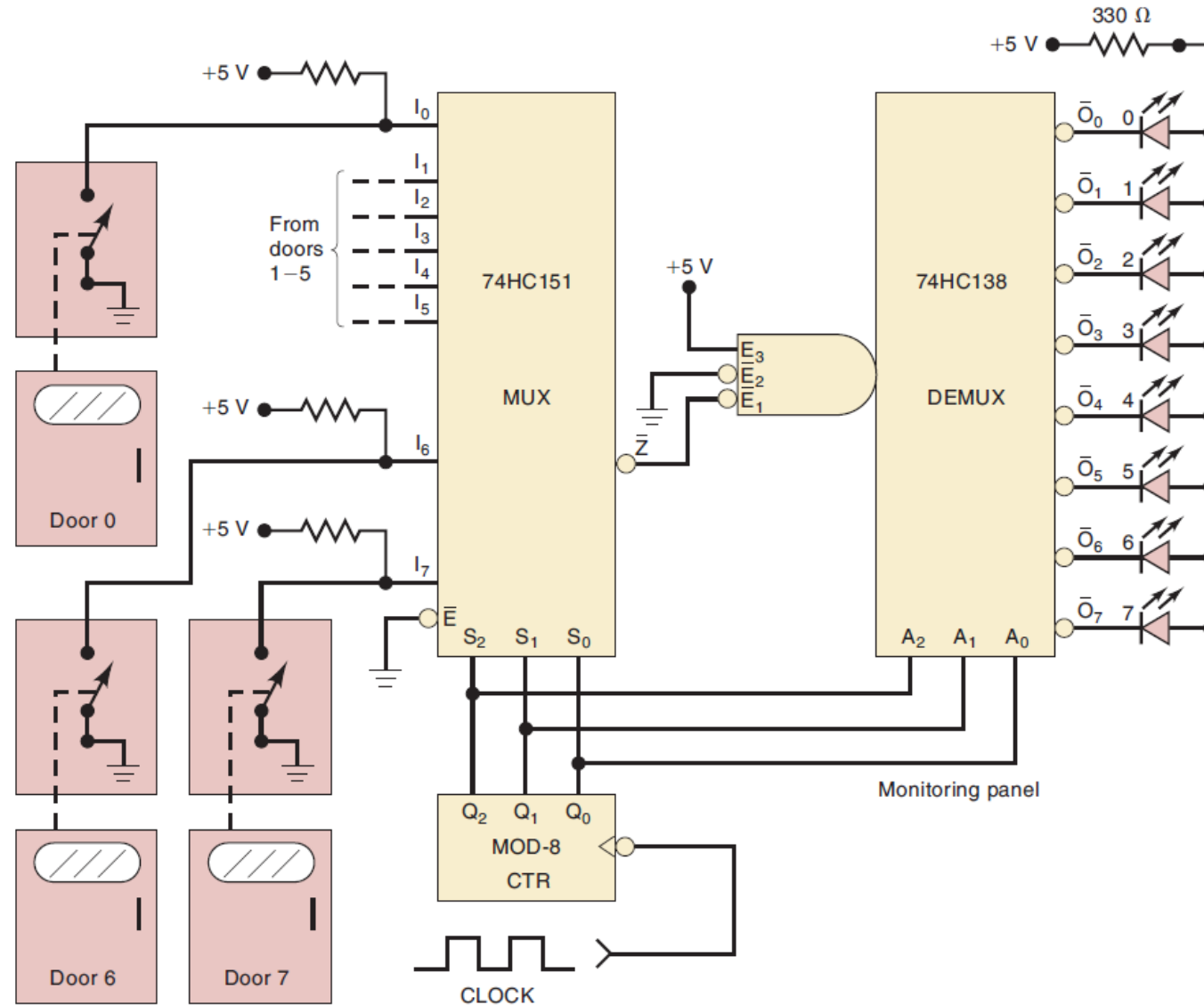

DECODER CIRCUIT

- A decoder receives a set of inputs representing a binary number and activates only the output that corresponds to that input number.

0010 → ② →

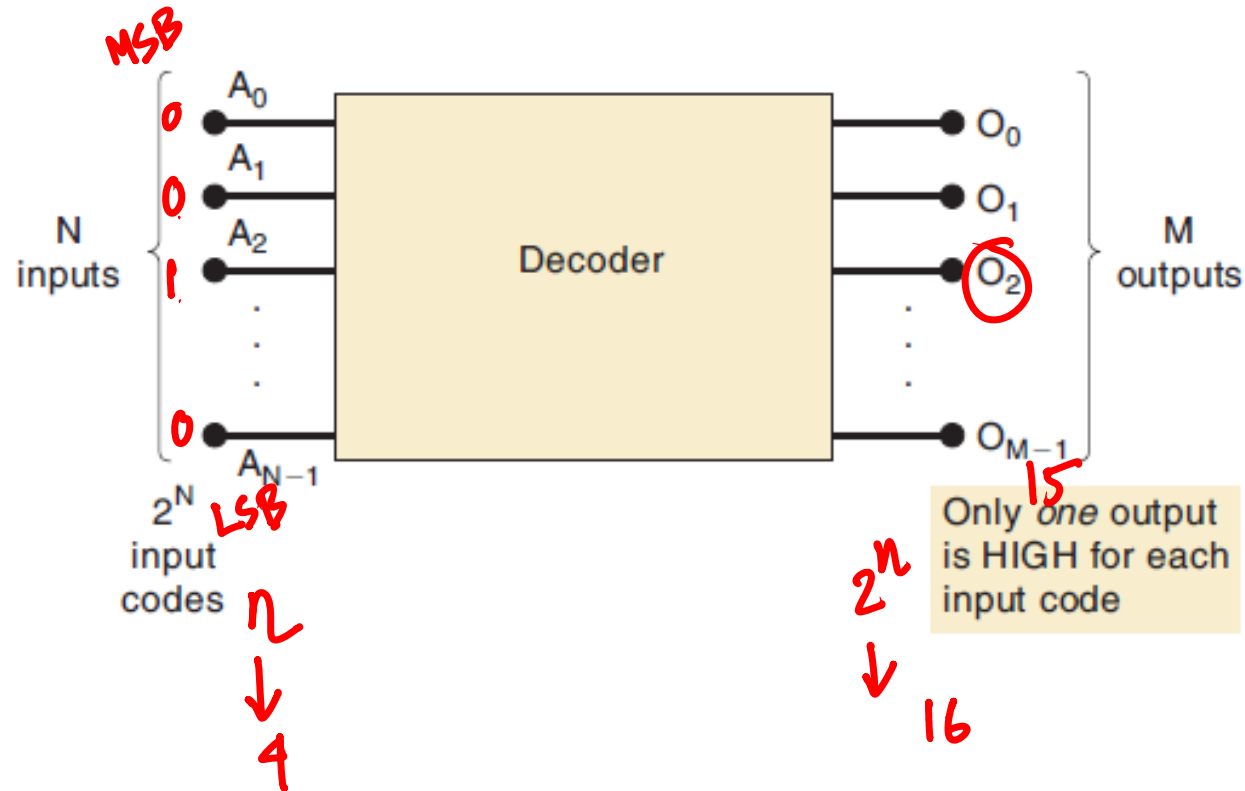


DECODER CIRCUIT

- 3-line-to-8-line decoder:

$\downarrow n$ $\downarrow 2^n$



	C	B	A	O ₇	O ₆	O ₅	O ₄	O ₃	O ₂	O ₁	O ₀
0 →	0	0	0	0	0	0	0	0	0	0	1
	0	0	1	0	0	0	0	0	0	1	0
3 →	0	1	0	0	0	0	0	0	1	0	0
	0	1	1	0	0	0	0	1	0	0	0
	1	0	0	0	0	0	1	0	0	0	0
6 →	1	0	1	0	0	1	0	0	0	0	0
	1	1	0	0	1	0	0	0	0	0	0
7 →	1	1	1	1	0	0	0	0	0	0	0

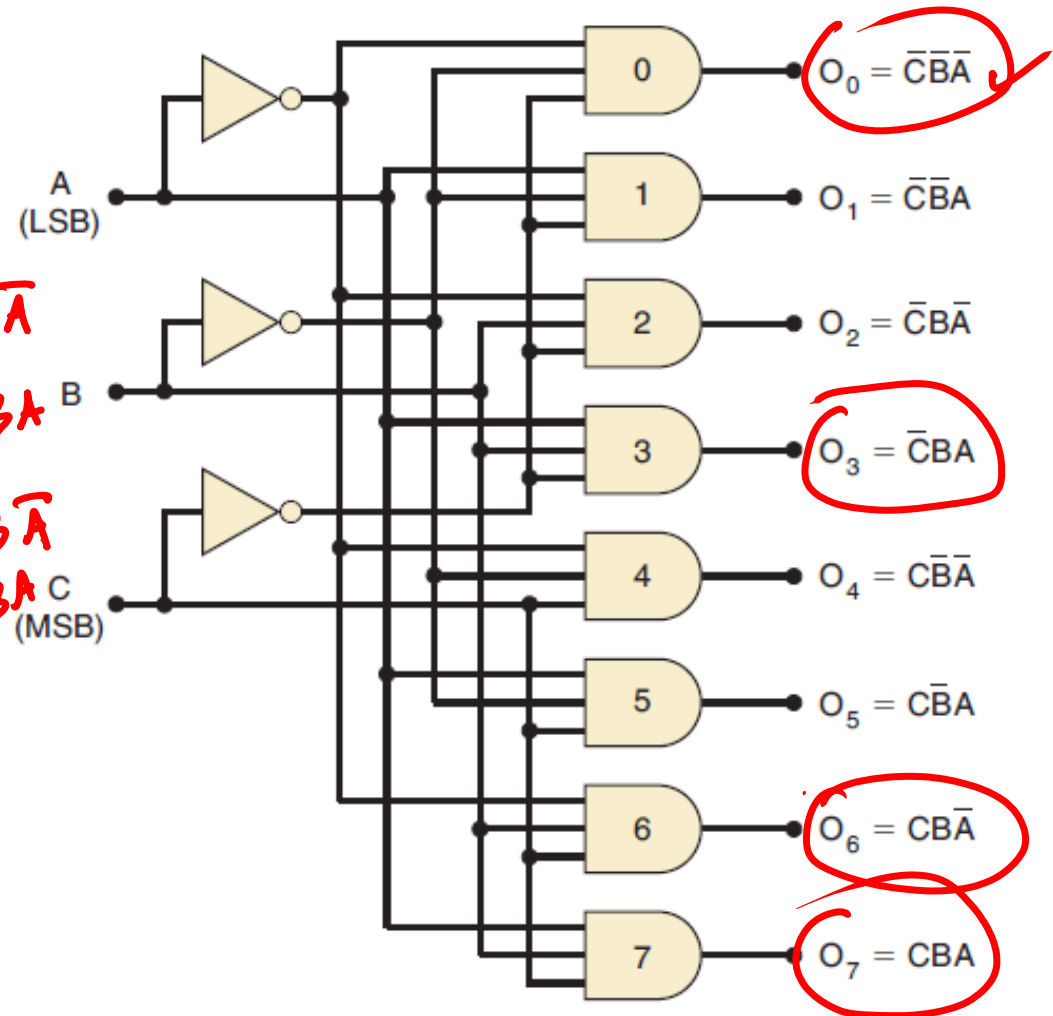$\textcircled{1} O_0 = \bar{C}\bar{B}\bar{A}$
 $O_3 = \bar{C}BA$
 $O_6 = C\bar{B}\bar{A}$
 $O_7 = CBA$





DECODER CIRCUIT

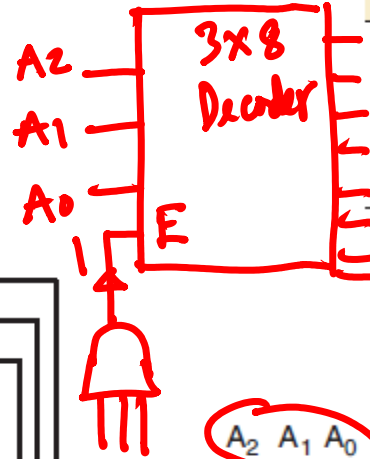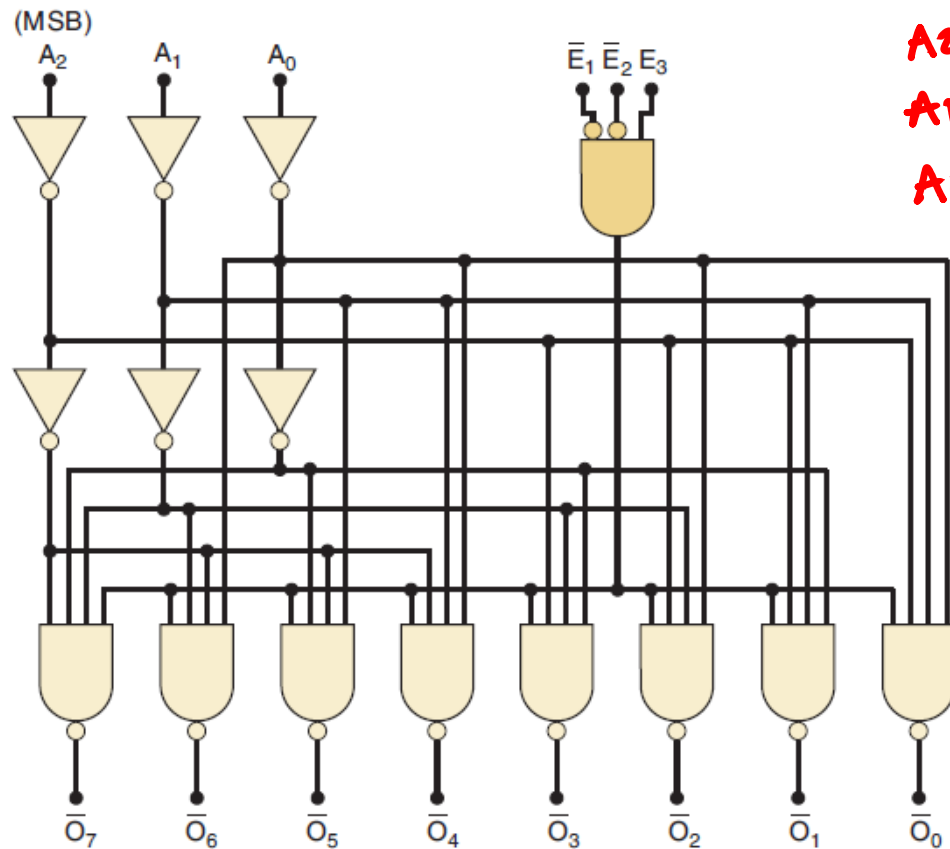- 3-line-to-8-line decoder with enable input:





\bar{E}_1	\bar{E}_2	E_3	Outputs
0	0	1	Respond to input code $A_2A_1A_0$
1	X	X	Disabled – all HIGH
X	1	X	Disabled – all HIGH
X	X	0	Disabled – all HIGH

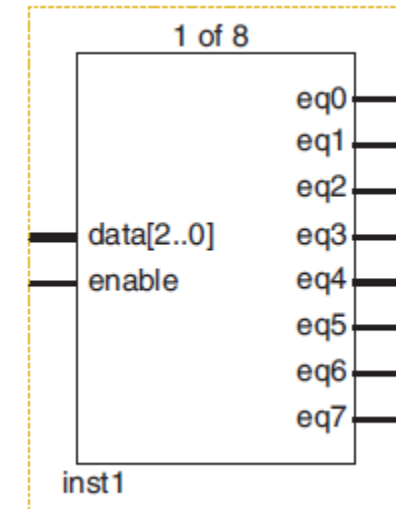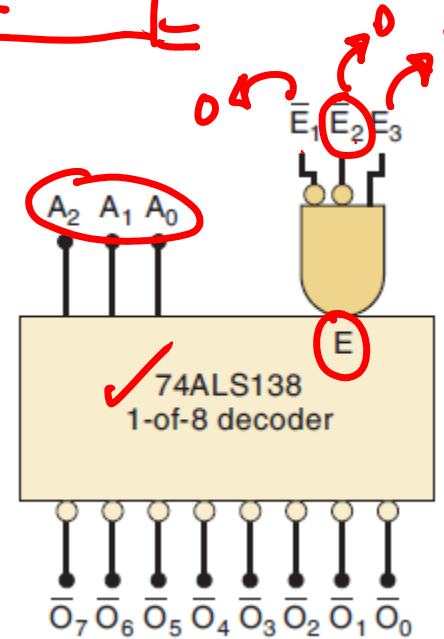


DECODER CIRCUIT

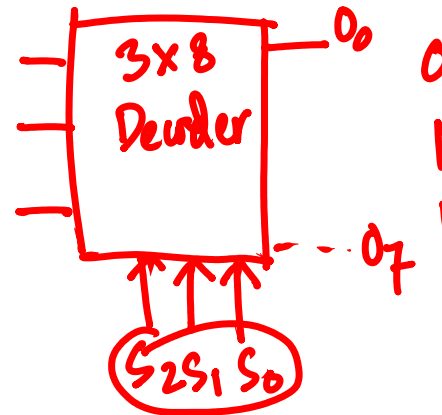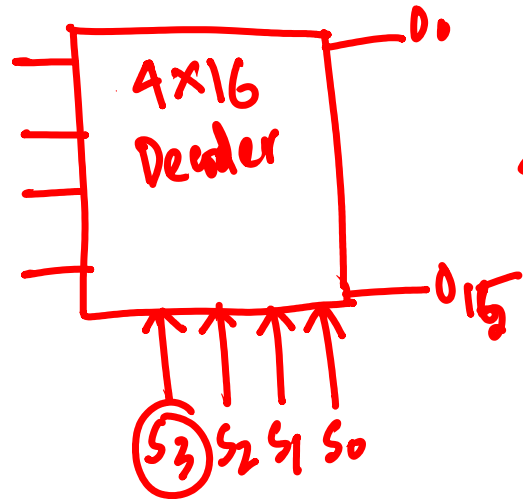- 4-line-to-16-line decoder with 3-line-to-8-line decoder :




w	
0	$D_0 - D_7$ (Dec 1)
1	$D_8 - D_{15}$ (Dec 2)

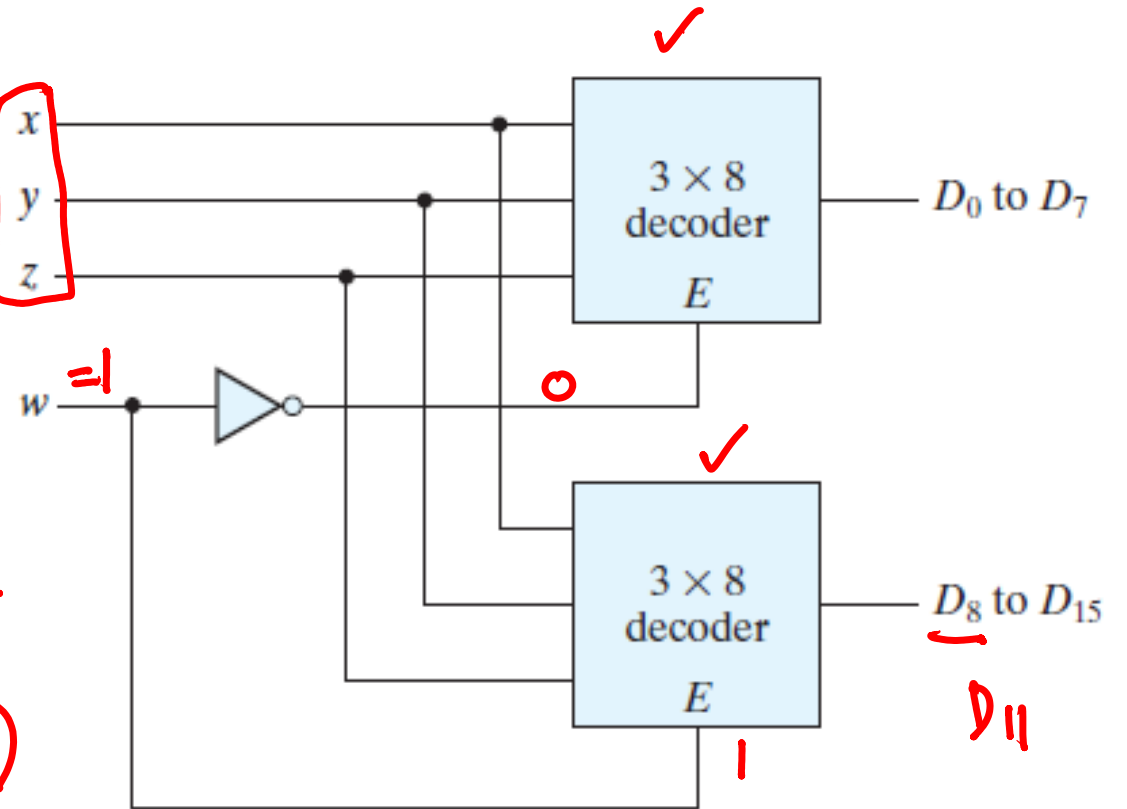

DECODER CIRCUIT

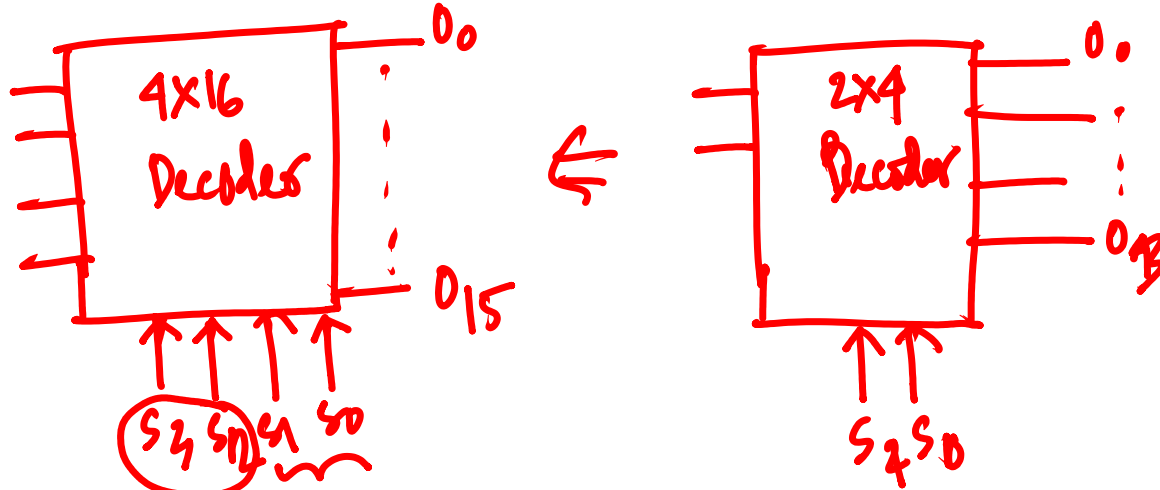- 4-line-to-16-line decoder with decoder tree:



Handwritten notes indicating input values for the decoder tree:

$W_3 = 1$, $W_2 = 0$
 $W_1 = 1$, $W_0 = 0$

W_3	W_2	$y_i \rightarrow$
0	0	$y_0 \rightarrow \text{Dec 1}$
0	1	$y_1 \rightarrow \text{Dec 2}$
1	0	$y_2 \rightarrow \text{Dec 3}$
1	1	$y_3 \rightarrow \text{Dec 4}$

